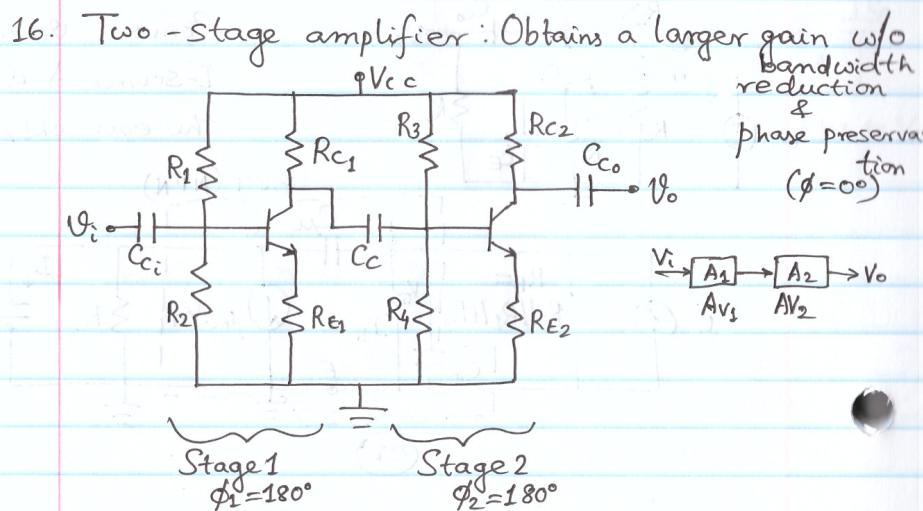



$$f_{3\text{db}} = \frac{1}{2\pi (R_B || r_{pi})(C_{pi} + C_M)}$$

(BJT)
ext. ckt.


(LPF like)



17. Equivalent 2-port networks:

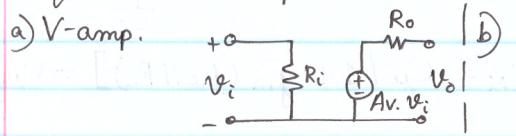


$V_{in} \rightarrow V_{out}$

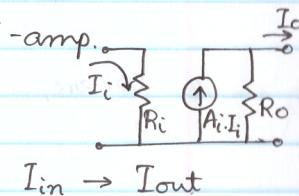


$I_{in} \rightarrow I_{out}$

c) Transconductance amp.

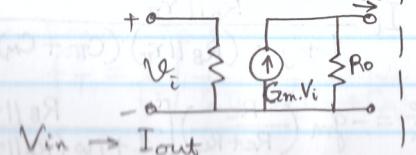

$V_{in} \rightarrow I_{out}$

d) Transresistance amp.

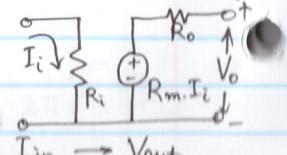

$I_{in} \rightarrow V_{out}$

Tutorial (BJTs)

1. Calculate β , α & I_c if $I_B = 10.2\mu A$ & $I_E = 0.9mA$

Soln: $I_E = (1+\beta) I_B$

$$\Rightarrow \beta = \frac{I_E}{I_B} - 1 = \frac{0.9 \times 10^{-3}}{10.2 \times 10^{-6}} - 1 = 87.23 \quad (\text{Ans})$$

Now, $\alpha = \frac{\beta}{1+\beta} = \frac{87.23}{87.23+1} = 0.988 \quad (\text{Ans})$

And, $I_c = \alpha \cdot I_E = (0.988)(0.9 \times 10^{-3}) = 0.889 \text{ mA} \quad (\text{Ans})$

2. Find r_o if $V_A = 190V$ & $I_c = 2.2 \text{ mA}$

Soln: $r_o = \frac{V_A}{I_c} = \frac{190}{2.2 \times 10^{-3}} = 86.363 \text{ k}\Omega \quad (\text{Ans})$

3. Find I_c at $V_{CE} = 12V$. Given, $I_c = 1.3 \text{ mA} @ V_{CE} = 1.5V$ & $V_A = 200V$. Assume $V_{BE(on)}$ is constant.

Soln: We know, $I_c = [I_s \cdot (e^{\frac{V_{BE}}{V_T}})] \left(1 + \frac{V_{CE}}{V_A}\right) = I_o \cdot \left(1 + \frac{V_{CE}}{V_A}\right)$


$$\Rightarrow 1.3 \times 10^{-3} = I_o \cdot \left(1 + \frac{1.5}{200}\right)$$

$$\Rightarrow I_o = 1.29 \times 10^{-3} \text{ A}$$

At $V_{CE} = 12V$,

$$I_c = 1.29 \times 10^{-3} \left(1 + \frac{12}{200}\right)$$
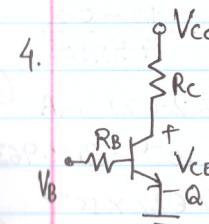
$$= 1.367 \text{ mA} @ V_{CE} = 12V \quad (\text{Ans})$$



Let, $V_{cc} = 5V$, $V_B = 2.2V$, $R_C = 4.2k\Omega$,

$R_B = 220k\Omega$, $\beta = 150$, $V_{BE(on)} = 0.7V$.

Calculate I_B , I_c , V_{CE} & $P_{transistor}$.


Solⁿ. $I_B = \frac{V_B - V_{BE(on)}}{R_B} = \frac{2.2 - 0.7}{220 \times 10^3} = 6.818 \mu A$ (Ans)

$$I_C = \beta \cdot I_B = 6.818 \times 10^{-6} \times 150 = 1.022 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C \cdot R_C = 5 - [(1.022 \times 10^{-3})(4.2 \times 10^3)]$$

$$= 0.707 \text{ V, Forward active mode}$$
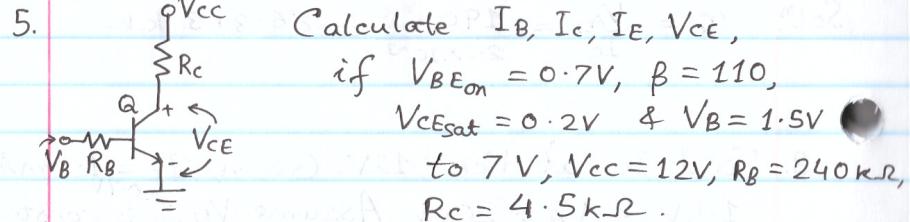
$$\begin{aligned} P_{\text{transistor}} &= I_B \cdot V_{BE(on)} + I_C \cdot V_{CE} \\ &= (6.818 \times 10^{-3})(0.7) + (1.022 \times 10^{-3})(0.707) \\ &= 5.495 \text{ mW} \end{aligned}$$



Solⁿ. $I_B = \frac{V_B - V_{BE(on)}}{R_B} = \frac{1.5 - 0.7}{240 \times 10^3} = 3.333 \mu A$ (Ans)

$$@V_B = 7 \text{ V} \quad I_B = \frac{7 - 0.7}{240 \times 10^3} = 26.25 \mu A$$

$$I_{C_{1.5V}} = \beta \cdot I_B = 110 \times 3.333 \times 10^{-6} = 366.63 \mu A$$


$$V_{CE} = V_{CC} - I_C \cdot R_C \Rightarrow V_{CE} > 0.2 \text{ V}$$

likely
 $I_{C_{7V}} \Rightarrow$ Transistor is in saturation mode.

$$\therefore I_{C_{7V}} = \frac{V_{CC} - V_{CEsat}}{R_C} = \frac{12 - 0.2}{4.5 \times 10^3} = 2.622 \mu A$$

$$I_{E_{1.5V}} = (1+\beta) I_B = (1+110) 3.333 \times 10^{-6} = 369.963 \mu A$$
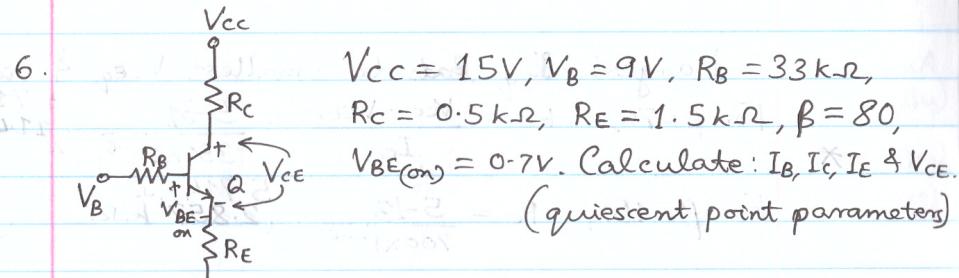
$$I_{E_{7V}} = I_B + I_C = 26.25 \times 10^{-6} + 2.622 \times 10^{-3} = 2.648 \text{ mA}$$




Solⁿ. $I_B = \frac{V_B - V_{BE(on)}}{R_B + (1+\beta) R_E} = \frac{9 - 0.7}{33 \times 10^3 + (1+80) \times 1.5 \times 10^3} = 53.721 \mu A$ (Ans)

$$I_C = \beta \cdot I_B = 80 \times 53.721 \times 10^{-6} = 4.297 \text{ mA}$$

$$I_E = (1+\beta) I_B = (1+80) \times 53.721 \times 10^{-6} = 4.351 \text{ mA}$$
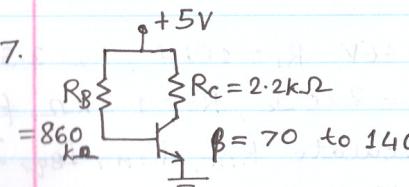
$$V_{CE} = V_{CC} - I_C \cdot R_C - I_E \cdot R_E = 15 - (4.297 \times 10^{-3})(0.5 \times 10^3) - (4.351 \times 10^{-3})(1.5 \times 10^3) = 6.325 \text{ V}$$



What is the actual range of V_{CEq} for the new R_C ?

Solⁿ. Assume, $V_{BE(on)} = 0.7 \text{ V}$ (s.) $I_{Bq} = \frac{V_{CC} - V_{BE(on)}}{R_B} = \frac{5 - 0.7}{860 \times 10^3} = 5 \mu A$

$$\text{For } \beta = 70, I_{Cq} = \beta \cdot I_{Bq} = 70 \times 5 \times 10^{-6} = 350 \mu A$$

$$\text{For } \beta = 140, I_{Cq} = 140 \times 5 \times 10^{-6} = 700 \mu A$$

Largest I_{CQ} leads to smallest V_{CEQ} & vice-versa
 For $\beta = 70$, $R_C = \frac{V_{CC} - V_{CEQ}}{I_{CQ}} = \frac{5-3}{\frac{350 \times 10^{-6}}{I_{CQ}}} = 5.714 k\Omega$ (Ans)

For $\beta = 140$, $R_C = \frac{5-1}{700 \times 10^{-6}} = 5.714 k\Omega$ (Ans)


Nominal $I_{CQ} = \frac{350 \times 10^{-6} + 700 \times 10^{-6}}{2} = 525 \mu A$

Nominal $V_{CEQ} = \frac{1+3}{2} = 2 V$

Nominal $R_C = \frac{V_{CC} - V_{CEQ_{nom.}}}{I_{CQ}} = \frac{5-2}{525 \times 10^{-6}} = 5.714 k\Omega$

For $I_{CQ} = 350 \mu A$, $V_{CEQ} = V_{CC} - I_{CQ} \cdot R_C$
 $(@ \beta = 70)$
 $= 5 - [350 \times 10^{-6}] (5.714 \times 10^3) = 3 V$ (Ans)

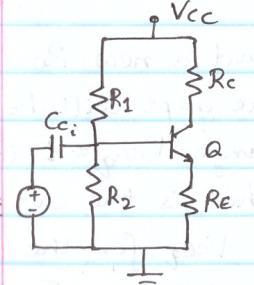For, $I_{CQ} = 700 \mu A$, $V_{CEQ} = 5 - [(700 \times 10^{-6}) (5.714 \times 10^3)] = 1 V$ (Ans)



$V_{CC} = 6V$, $R_1 = 10k\Omega$, $R_2 = 2.5k\Omega$,
 $R_E = 220\Omega$, $R_C = 1.2k\Omega$, $\beta = 160$.
 Calculate R_{TH} , V_{TH} , I_{BQ} , I_{CQ} , & V_{CEQ} .

Soln.

$$R_{TH} = R_1 \parallel R_2 = \frac{10k \times 2.5k}{10k + 2.5k} = 2k\Omega \quad (\text{Ans})$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} \cdot V_{CC} = \frac{2.5k}{10k + 2.5k} \times 6 = 1.2V \quad (\text{Ans})$$

$$I_{BQ} = \frac{V_{TH} - V_{BEon}}{R_{TH} + (1+\beta)R_E} = \frac{1.2 - 0.7}{2 \times 10^3 + (1+160) \times 220} = 13.361 \mu A \quad (\text{Ans})$$


Assume, $V_{BEon} = 0.7V$

$$I_{CQ} = \frac{V_{TH} - V_{BEon}}{R_{TH} + (1+\beta)R_E} = \frac{1.2 - 0.7}{2 \times 10^3 + (1+160) \times 220} = 13.361 \mu A \quad (\text{Ans})$$

$$I_{EQ} = \beta \cdot I_{BQ} = 160 \times 13.361 \times 10^{-6} = 2.137 mA \quad (\text{Ans})$$

$$I_{EQ} = (1+\beta) I_{BQ} = 2.151 mA \quad (\text{Ans})$$
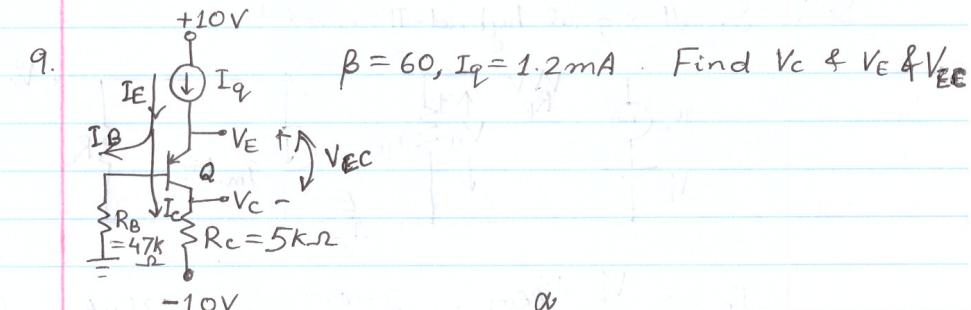
$$V_{CEQ} = V_{CC} - I_{CQ} \cdot R_C = 6 - [(2.137 \times 10^{-3})(1.2 \times 10^3)] = 2.960 V \quad (\text{Ans})$$



Soln.

$$I_E = 1.2 mA; I_C = \left(\frac{\beta}{1+\beta} \right) I_E = \frac{50}{1+50} \times 1.2 \times 10^{-3} = 1.176 mA$$


$$V_C = I_C \cdot R_C + V_{EE} = (1.176 \times 10^{-3}) (5 \times 10^3) - 10 = -3.12V \quad (\text{Ans})$$

$$I_B = \frac{I_C}{\beta} = \frac{1.176 \times 10^{-3}}{60} = 19.6 \mu A$$

$$V_E = I_B \cdot R_B + V_{BEon} = (19.6 \times 10^{-6}) (47 \times 10^3) + 0.7 = 1.621 V \quad (\text{Ans})$$


$$V_{EC} = V_E - V_C = 1.621 - (-3.12) = 4.74 V \quad (\text{Ans})$$

10.

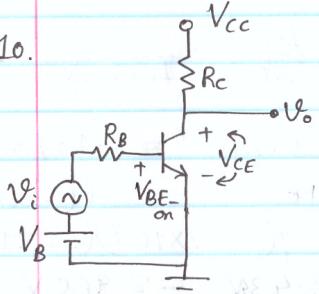

$V_{cc} = 6V$, $V_B = 2V$, $R_B = 640k\Omega$,
 $R_c = 12k\Omega$, $V_{BEon} = 0.7V$, $\beta = 90$.
Draw the small signal hybrid- π model. Find g - p t values, g_m , r_{π} .
Calculate small-signal V -gain.

Soln. Small signal hybrid- π model:

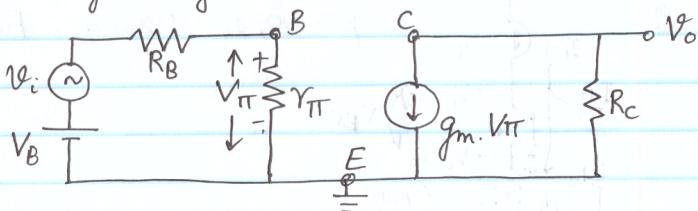

$$I_{Bq} = \frac{V_B - V_{BEon}}{R_B} = \frac{2 - 0.7}{640 \times 10^3} = 2.031 \mu A \quad (\text{Ans})$$

$$I_{Cq} = \beta \cdot I_{Bq} = 90 \times 2.031 \times 10^{-6} = 182.812 \mu A \quad (\text{Ans})$$

$$V_{CEq} = V_{cc} - I_{Cq} \cdot R_c = 6 - [182.812 \times 10^{-6} \times 12 \times 10^3] = 3.806 V$$

$$I_{Eg} = I_{Bq} + I_{Cq} = 2.031 \mu A + 182.812 \mu A = 184.843 \mu A \quad (\text{Ans})$$

$$g_m = \frac{I_{Cq}}{V_T} = \frac{182.812 \times 10^{-6}}{0.026} = 7.031 \text{ mA/V} \quad (\text{Ans})$$

Assume $V_T = 26 \text{ mV}$


$$r_{\pi} = \frac{\beta \cdot V_T}{I_{Cq}} = \frac{90 \times 0.026}{182.812 \times 10^{-6}} = 12.800 k\Omega \quad (\text{Ans})$$

$$\frac{V_o}{V_i} = A_v = -g_m \cdot R_c \left(\frac{r_{\pi}}{r_{\pi} + R_B} \right) \quad [\because A_v = -g_m \cdot r_{\pi} \cdot R_c]$$

$$= -(7.031 \times 10^{-3}) \times (12 \times 10^3) \times \left(\frac{12.8 \times 10^3}{12.8 \times 10^3 + 640 \times 10^3} \right)$$

$$= -1.654 \leftarrow \text{No unit}$$

11.

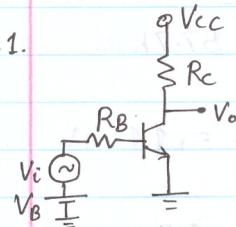

$V_{cc} = 7V$, $V_B = 1V$, $V_A = 200V$, $\beta = 120$,
 $R_c = 15k\Omega$, $V_{BEon} = 0.7V$, $R_B = 120k\Omega$.
Calculate g_m , r_{π} , r_o & A_v .

$$\text{Soln. } g_m = \frac{I_{Cq}}{V_T} = \frac{\beta \cdot I_{Bq}}{V_T} = \frac{\beta \cdot (V_B - V_{BEon})}{R_B \cdot V_T}$$

$$= \frac{120 \times \left(\frac{1 - 0.7}{120 \times 10^3} \right)}{0.026} = 11.538 \text{ mA/V} \quad (\text{Ans})$$

$$r_{\pi} = \frac{\beta \cdot V_T}{I_{Cq}} = \frac{120 \times 0.026}{120 \times \left(\frac{1 - 0.7}{120 \times 10^3} \right)} = 10.4 k\Omega \quad (\text{Ans})$$


$$r_o = \frac{V_A}{I_{Cq}} = \frac{200 \times 10^3}{0.3} = 666.666 k\Omega \quad (\text{Ans})$$

$$A_v = \frac{V_o}{V_i} = -g_m \left(\frac{r_{\pi}}{r_{\pi} + R_B} \right) (r_o / R_c)$$

$$= -(11.538 \times 10^{-3}) \left(\frac{10.4 k\Omega}{10.4 k\Omega + 120 k\Omega} \right) (666.666 k\Omega / 15 k\Omega)$$

$$= -13.499 \quad (\text{Ans})$$



12.

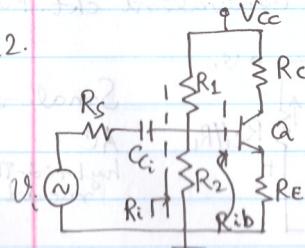

$V_{cc} = 5V$, $R_c = 5.6k\Omega$, $R_E = 0.6k\Omega$,
 $\beta = 120$, $R_1 = 250k\Omega$, $R_2 = 75k\Omega$, $V_A = \infty$,
 $R_s = 0.5k\Omega$ & $V_{BEon} = 0.7V$.

Find: R_{ib} & R_i .

r_o must be shown
in hybrid- π

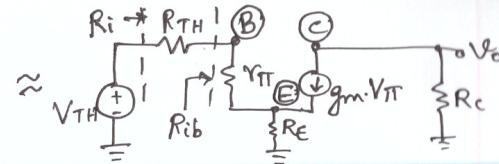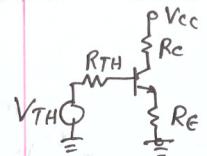

$$SOLN: R_{TH} = R_1 // R_2 = \frac{250k \times 75k}{250k + 75k} = 57.7k\Omega$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{75k}{75k + 250k} \cdot 5 = 1.154V$$

$$I_{Bq} = \frac{V_{TH} - V_{BEon}}{R_{TH} + (1+\beta)RE} = \frac{1.154 - 0.7}{57.7 - (120+i)(0.6k)} = 3.48\mu A$$

$$I_{Cq} = \beta \cdot I_{Bq} = 120 \times 3.48 \times 10^{-6} = 0.418mA$$

$$g_m = \frac{I_{Cq}}{V_T} = \frac{0.418 \times 10^{-3}}{0.026} = 16.08 \text{ mA/V}$$


$$r_\pi = \frac{\beta \cdot V_T}{I_{Cq}} = \frac{120 \times 0.026}{0.418 \times 10^{-3}} = 7.46 k\Omega$$

$$\times V_o = -g_m \cdot V_\pi \cdot R_C$$

$$R_{IB} = r_\pi + (1+\beta)RE = 7.46k\Omega + (1+120)(0.6 \times 10^3) = 80.1 k\Omega \quad (\text{Ans})$$



$$R_i = R_1 // R_2 + R_{IB} = 57.7k + 80.1k = 137.8 k\Omega \quad (\text{Ans})$$

13.

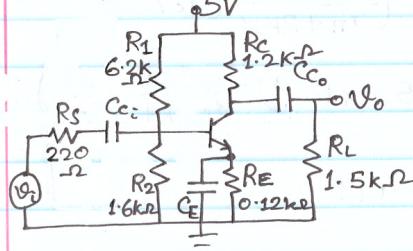

$\beta = 200, r_o = \infty$
Find small signal
hybrid- π parameters
after drawing an
equivalent ckt. Find A_v

SOLN.

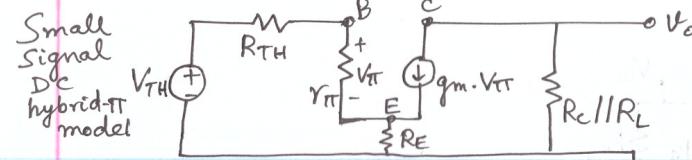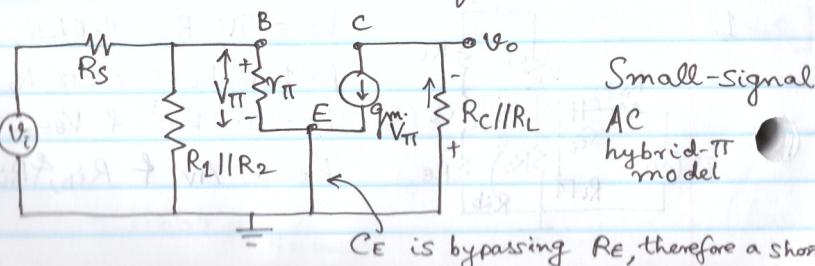

Assume,
 $V_{TR} = V_{BEon} = 0.7V$
 $\& V_T = 26 mV$

$$R_{TH} = R_1 // R_2 = \frac{6.2k \cdot 1.6k}{6.2k + 1.6k} = 1.271 k\Omega$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} \cdot V_{CC} = \frac{1.6k}{6.2k + 1.6k} \cdot 5 = 1.025V$$

$$I_{Bq} = \frac{V_{TH} - V_{BEon}}{R_{TH} + (1+\beta)RE} = \frac{1.025 - 0.7}{1.271k + (1+200)0.12k} = 12.799 \mu A$$

$$I_{Cq} = \beta \cdot I_{Bq} = 200 \times 12.799 \times 10^{-6} = 2.559mA \quad (\text{Ans})$$

$$I_{Cq} = (1+\beta)I_{Bq} = 2.572mA$$


$$V_{CEq} = V_{CC} - I_{Cq} \cdot R_C - I_{Eq} \cdot R_E = 5 - (2.559m)(1.2k) - (2.572m)(0.12k) = 1.620V \quad (\text{Ans})$$

$$r_\pi = \frac{\beta \cdot V_T}{I_{Cq}} = \frac{200 \times 0.026}{2.559 \times 10^{-3}} = 2.032 k\Omega \quad (\text{Ans})$$

$$g_m = \frac{I_{Cq}}{V_T} = \frac{2.559 \times 10^{-3}}{0.026} = 98.423 \text{ mA/V} \quad (\text{Ans})$$

$$A_v = -g_m \cdot \left[\frac{R_1 // R_2 // r_\pi}{(R_1 // R_2 // r_\pi) + R_s} \right] (R_C // R_L)$$
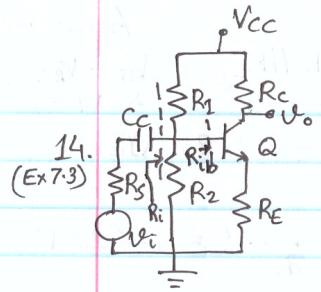
$$= -98.423m \left[\frac{6.2k // 1.6k // 2.032k}{(6.2k // 1.6k // 2.032k) + 220} \right] (1.2k // 1.5k) \quad (\text{Ans})$$



14.
(Ex 7.3)

$$R_S = 0.1 \text{ k}\Omega, R_1 = 20\text{k}, R_2 = 2.2\text{k}, R_E = 0.1\text{k}, R_C = 2\text{k}, C_C = 47\mu\text{F}, V_{CC} = 10\text{V}, V_{BEon} = 0.7\text{V}, \beta = 200, V_A = \infty.$$

Find τ_s & f_c & A_v mid-band.

Solⁿ.

$$\tau_s = (R_i + R_S) \cdot C_C$$

$$f_c = \frac{1}{2\pi \tau_s}$$

$$R_{TH} = R_1 // R_2 = \frac{20\text{k} \cdot 2.2\text{k}}{20\text{k} + 2.2\text{k}} = 1.98\text{k}\Omega$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} \cdot V_{CC} = \frac{2.2\text{k}}{20\text{k} + 2.2\text{k}} \cdot 10 = 0.990\text{V}$$

$$I_{BQ} = \frac{V_{TH} - V_{BEon}}{R_{TH} + (1+\beta)R_E} = \frac{0.990 - 0.7}{1.98\text{k} + (1+200)0.1\text{k}} = 13.2\mu\text{A}$$

$$I_{CQ} = \beta \cdot I_{BQ} = 200 \cdot 13.2\mu = 2.636\text{mA}$$

$$r_\pi = \frac{\beta \cdot V_T}{I_{CQ}} = \frac{200 \times 0.026}{2.636\text{mA}} = 1.97\text{k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{2.636\text{mA}}{0.026} = 101.4\text{mA/V}$$

$$R_{ib} = r_\pi + (1+\beta) \cdot R_E = 1.97\text{k} + (1+200)0.1\text{k} = 22.1\text{k}\Omega$$

$$R_B = R_1 // R_2 = 1.98\text{k}\Omega$$

$$R_i = R_B // R_{ib} = \frac{1.98\text{k} \cdot 22.1\text{k}}{1.98\text{k} + 22.1\text{k}} = 1.817\text{k}\Omega$$

$$\therefore \tau_s = (R_i + R_S) \cdot C_C = (1.817\text{k} + 0.1\text{k}) \cdot 47\mu = 90.099\text{ms}$$

(Ans)

$$f_c = \frac{1}{2\pi \tau_s} = \frac{1}{2\pi \times 90.099\text{ms}} = 1.77\text{Hz}$$


(High pass)
(Ans)

$$A_v \text{ mid-band} = \frac{-\beta \cdot R_C}{r_\pi + (1+\beta)R_E} \cdot \frac{R_i}{R_i + R_S}$$

$$= \frac{-(200)(2\text{k})}{1.97\text{k} + (1+200)0.1\text{k}} \cdot \frac{1.817\text{k}}{1.817\text{k} + 0.1\text{k}}$$

(Ans)

DC hybrid- π model: Small-signal

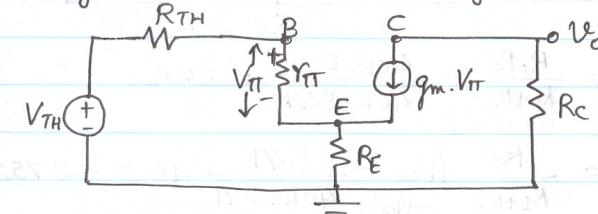

AC hybrid- π model: Small Signal

