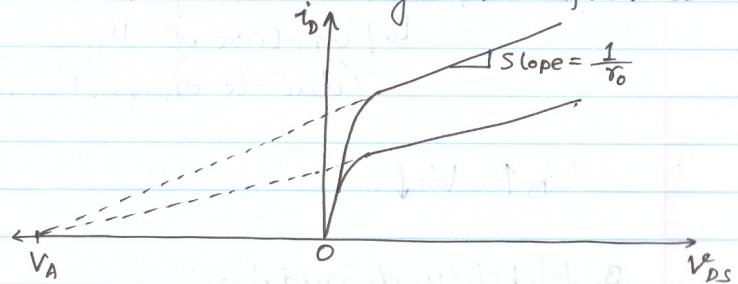


Advantages of CMOS: or MOSFETS

- 1. Compact
 - 2. Low power
 - 3. Robust
 - 4. High density fabrication.

h. Non-ideal MOSFET characteristics:

i) V-I characteristics gets modified due to V_A .



In saturation region

$$i_D = K_n [(V_{GS} - V_{TN})^2 \cdot (1 + \lambda \cdot V_{DS})]$$

where, ~~what~~ ~~when~~ ~~why~~ ~~how~~ it looks like

$\lambda \Rightarrow$ Channel length modulation parameter.


$$\therefore r_o = \frac{1}{\lambda \cdot I_{Dq}} = \frac{V_A}{I_{Dq}} \quad (\text{O/P resistance})$$

$$V_A = \frac{1}{\lambda} \text{ (Abstand 3,5 m mit 25 m/s)}$$

ii) Short channel effects:

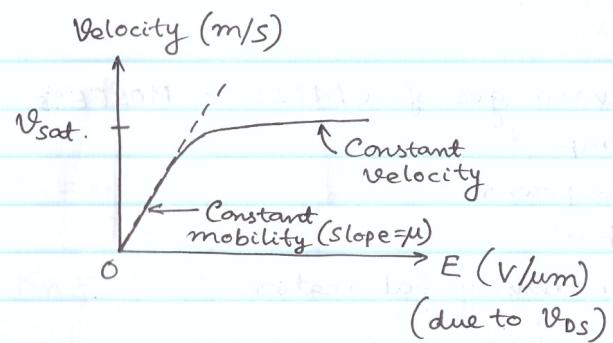1. Velocity saturation.

$V_{DS} \uparrow$ $E_{DS}^{\text{f}} \uparrow$ Velocity of carrier
 (horizontal) (upto a limit of V_{DS})



2. Threshold voltage variation:

- $V_T \rightarrow$ Function of 'L' (directly proportional)
- \hookrightarrow Function of V_{DS} (due to channel length modulation)

$$V_{DS} \uparrow \quad V_T \downarrow$$

3. Mobility degradation:


$$\frac{V_{GS}}{V_{SG}} \uparrow \quad E_{\text{vertical}} \uparrow \quad \mu \downarrow$$

(related to velocity saturation).

iii) Body effect & substrate biasing:

A single substrate is shared among multiple MOSFETs (eg. two n-ch). This causes threshold voltage variation in some MOSFETs as compared to others of same type.

i) Common source (DC) ckt: 2NMOS

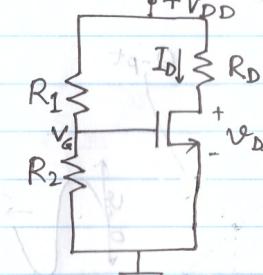


$$V_G = V_{GS} = \frac{R_2}{R_1 + R_2} \cdot V_{DD}$$

$$I_D = K_n (V_{GS} - V_{Tn})^2 \quad (\text{Saturation})$$


$$V_{DS} = V_{DD} - I_D \cdot R_D$$

$$P_T = V_{DS} \cdot I_D$$

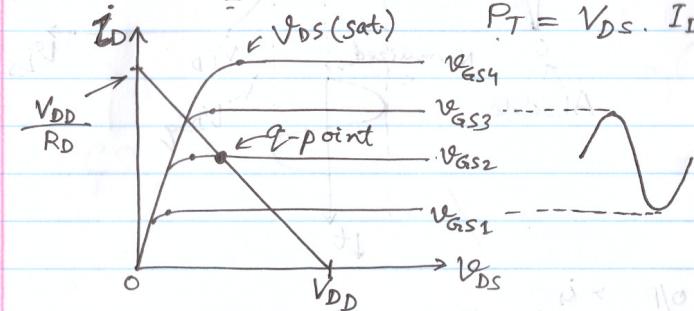


j) MOSFET as other electrical components:


1. Capacitor: MOS capacitor

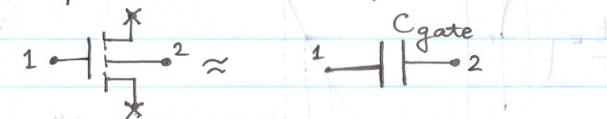


2. Resistor


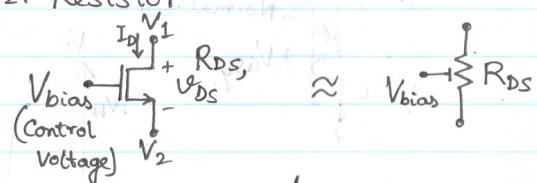


3. Diode

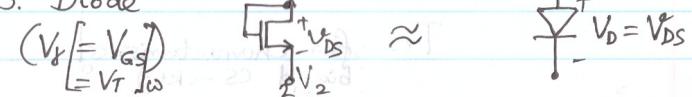


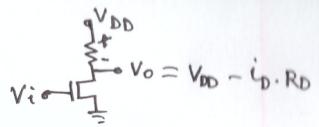

k. MOSFET amplifier: Common Source

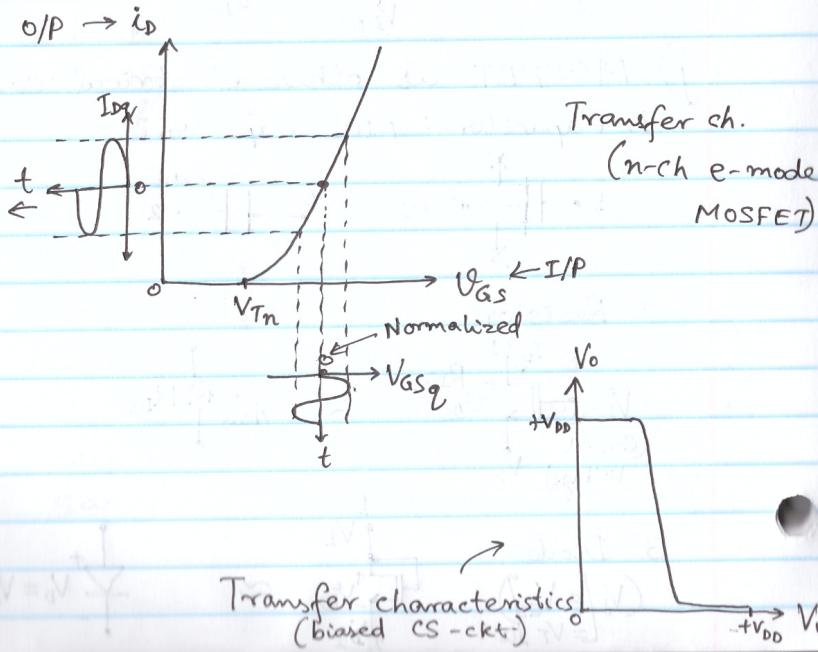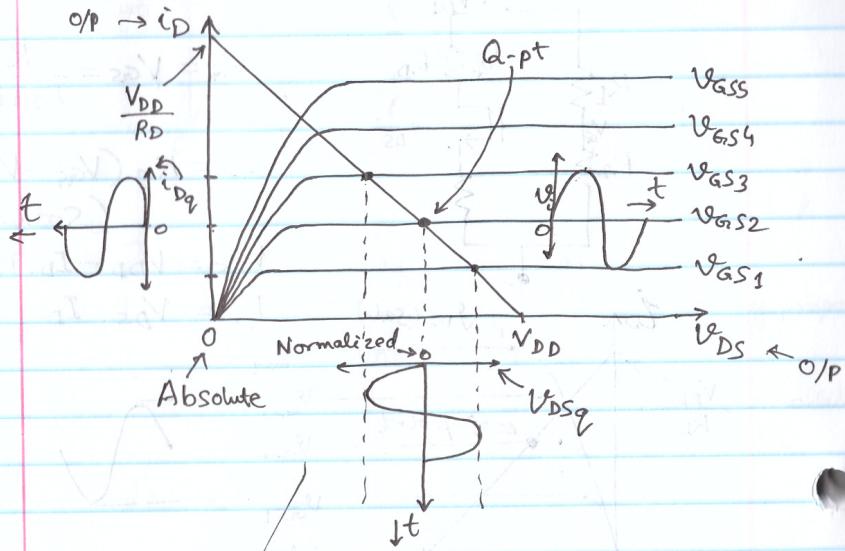


l. Small signal equivalent ckt: AC

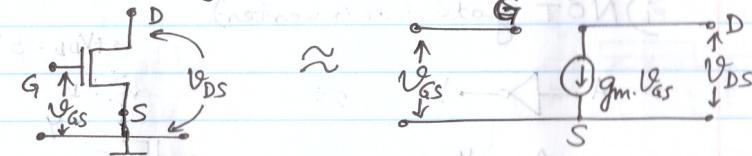

$$g_m = \left. \frac{\partial i_D}{\partial v_{AS}} \right|_{V_{AS} = V_{ASq} = \text{constant}}$$

$$g_m = 2 \sqrt{K_n \cdot I_{Dq}} = 2 \cdot K_n (V_{GSq} - V_{TN})$$

m. CS amplifier with S-resistor(R_s)

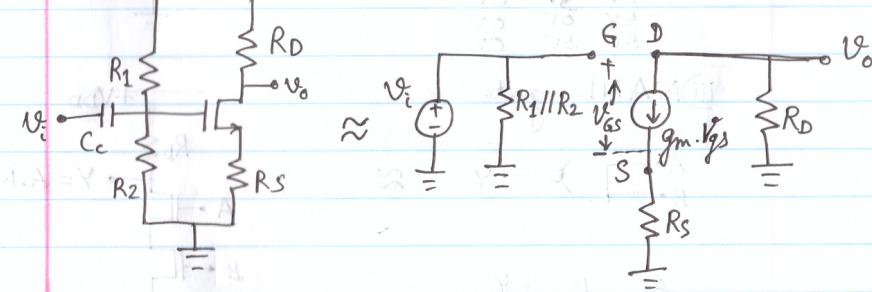

$$V_o = -q_m \cdot V_{GS} \cdot R_D$$



$$V_i = V_{gs} + (gm \cdot V_{gs}) R_s = V_{gs}(1 + gm \cdot R_s)$$

$$A_V = \frac{V_o}{V_i} = -\frac{g_m \cdot R_D}{1 + g_m \cdot R_S} \approx -\frac{R_D}{R_S}$$



(∴ gm is large)

m. Digital circuits using MOSFETs:



i) NOT gate (or inverter)

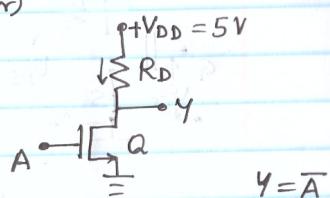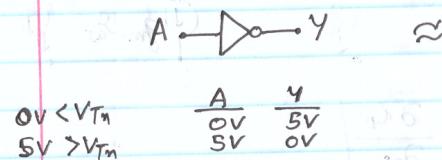

ii) NOR gate:

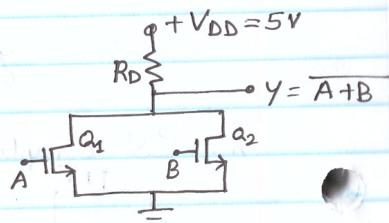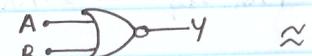

iii) NAND gate:

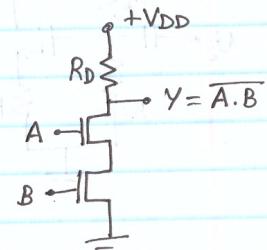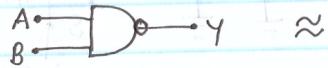

A	B	Y
0V	0V	5V
0V	5V	5V
5V	0V	5V
5V	5V	0V


OV: Logic '0'
5V: Logic '1' (or $+V_{DD}$)

($V_{GS} > V_T$ & $V_{DS} < 0$) cut-off region


Normally-ON

n. Depletion-mode MOSFETs : n & p channels.



Structure

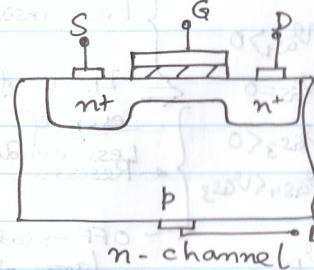

or

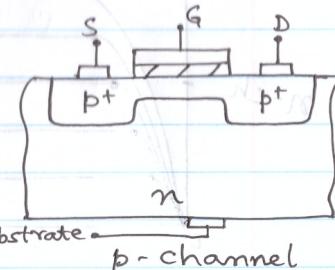


$$V_{Tn} < V_{GS} < 0$$

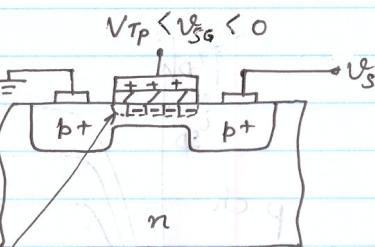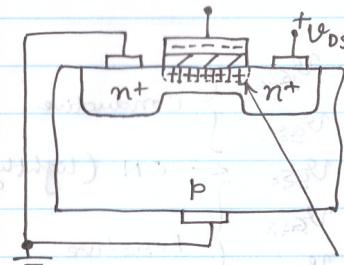

Depletion region
forms due to inversion
(blocks the channel)

At $V_{GS} \approx V_T$, the channel is completely blocked.
At $V_{GS} \approx 0$, " " " " " ON.

Symbols of depletion-mode MOSFETs:

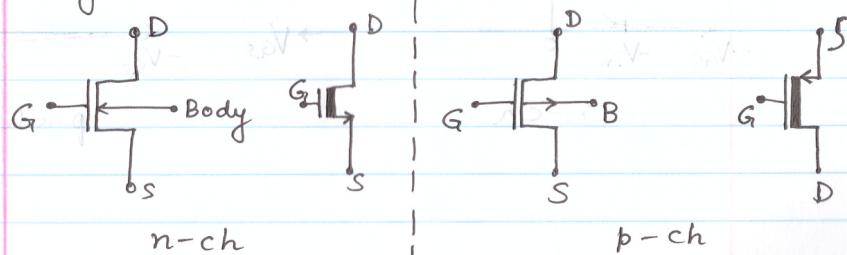

V-I characteristics (n-ch) & (p-ch)

$$V_{DS(\text{sat})} = V_{GS} - V_{Tn}$$

