

(8)

→ Combinatorial Circuits- Output = P , Input = x, y, z and $P = (x \text{ and } y) \text{ or } z'$ P is true when $\langle xyz \rangle = 000, 010, 100, 110, 111$ This is a combinatorial circuit. But in COA, we use sequential circuit- Now suppose, $p = (x+z') \cdot (y+z)$ Let $x=0; \Rightarrow P = z' \cdot (y+z) = z' \cdot y$

$$\therefore \boxed{\langle xyz \rangle = 010}$$

Let $x=1 \Rightarrow P = (y+z)$ Let $y=0 \Rightarrow z=1 \therefore \boxed{\langle xyz \rangle = 101}$ Let $y=1 \Rightarrow z=0 \text{ or } 1 \text{ both are sol}^n \therefore \boxed{\langle xyz \rangle = 110, 111}$ So total solⁿ $\Rightarrow \langle xyz \rangle = 010, 101, 110, 111$ - Let $q = x \cdot z' + y \cdot z \Rightarrow$ Input y, z ; output = q Giving no term
Hence only in two toIf $yz=11 \Rightarrow q=1$ $yz=00 \Rightarrow \underline{q}$ retain (Prev value of q is same as new value). $yz=01 \Rightarrow q=0$ $yz=10 \Rightarrow$ retain.

circuit

In switching ~~circuit~~ all inputs are initialised with true.

$$\therefore \text{In } q = q \cdot z' + y \cdot z$$

Step 1 $yz = 11 \Rightarrow q = 1$. Now yz is changed to 10.
 ~~$yz = 10$~~ and q is currently 1.

Step 2 ~~if~~ Now $\Rightarrow (\text{new } q) = (\text{old } q) \cdot z' + y \cdot z$
 \Rightarrow with $(\text{old } q) = 1$; $yz = 10$;

$$\underline{(\text{new } q) = 1}$$

Step 3 Now, yz is changed to 01; and $(\text{old } q) = 1$
 $\therefore (\text{new } q) = 0$

Step 4 Now, yz is changed to 00; $(\text{old } q) = 0$
 $\therefore \text{new } q = 0$