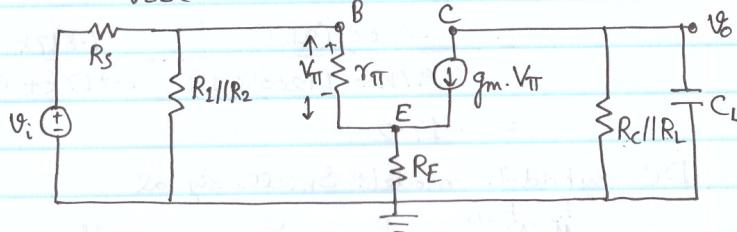


Find: I_C , hybrid- π model parameters, f_{BW} & corner frequencies.

Soln.



$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = \frac{40k \cdot 5.7k}{40k + 5.7k} = 5k\Omega$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} [V_{CC} - \frac{5.7k}{40k + 5.7k} \cdot 10] = -3.752V$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)} - V_{EE}}{R_{TH} + (1+\beta)R_E} = \frac{-3.752 - 0.7 + 5}{5k + (1+100) \cdot 0.5k} = 9.86 \mu A$$


$$I_{CQ} = \beta \cdot I_{BQ} = 100 \cdot 9.86 \mu A = 986 \mu A \quad (\text{Ans})$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{986 \mu A}{0.026} = 37.925 \text{ mA/V} \quad (\text{Ans})$$

$$r_\pi = \frac{\beta \cdot V_T}{I_{CQ}} = \frac{100 \times 0.026}{986 \mu A} = 2.637 k\Omega \quad (\text{Ans})$$

$$\tau_L = (R_L || R_2) C_L = \frac{5k \cdot 5k}{5k + 5k} \cdot 5 \text{ pF} = 12.5 \text{ ns}$$
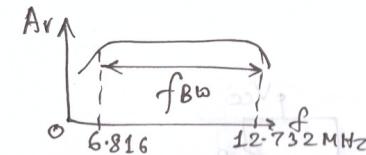
$$R_i = r_\pi + (1+\beta)R_E = 2.637 k\Omega + (1+100)0.5k\Omega = 53.137 k\Omega$$



$$\tau_S = (R_i || R_{TH} + R_s) C_C = \left(\frac{53.137k \cdot 5k}{53.137k + 5k} + 0.1k \right) \cdot 5\mu F = 23.349 \text{ ms}$$

$$\therefore f_L = \frac{1}{2\pi \tau_S} = \frac{1}{2\pi \times 23.349 \text{ ms}} = 6.816 \text{ Hz} \quad (\text{Ans})$$

$$\therefore f_H = \frac{1}{2\pi \tau_L} = \frac{1}{2\pi \times 12.5 \text{ ns}} = 12.732 \text{ MHz} \quad (\text{Ans})$$

$$f_{\text{bandwidth}} = f_H - f_L \approx 12.732 \text{ MHz} \quad (\text{Ans})$$

16. Ex 7.9 A BJT has $\beta_0 = 150$, $C_\pi = 2 \text{ pF}$, $C_\mu = 0.3 \text{ pF}$, $I_{CQ} = 0.5 \text{ mA}$, find f_B (bandwidth) & f_T (gain-bandwidth product).


Soln.

$$r_\pi = \frac{\beta_0 \cdot V_T}{I_{CQ}} = \frac{150 \times 0.026}{0.5 \text{ mA}} = 7.8 k\Omega$$

$$f_B = \frac{1}{2\pi r_\pi (C_\pi + C_\mu)} = \frac{1}{2\pi \times 7.8k (2p + 0.3p)} = 8.87 \text{ MHz} \quad (\text{Ans})$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.5 \text{ mA}}{0.026} = 19.23 \text{ mA/V}$$
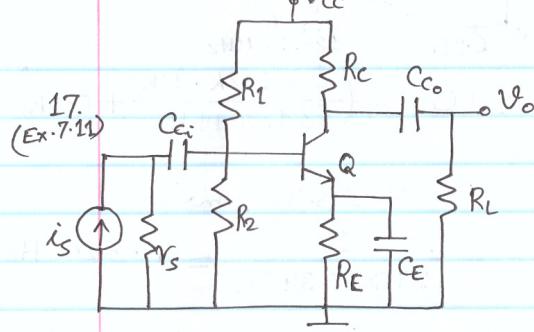
$$f_T = \frac{g_m}{2\pi (C_\pi + C_\mu)} = \frac{19.23 \text{ mA}}{2\pi (2p + 0.3p)} = 1.330 \text{ GHz} \quad (\text{Ans})$$




Draw the high-freq hybrid- π ckt.


$$R_1 = 200\text{k}\Omega, R_2 = 220\text{k}\Omega, R_C = 2.2\text{k}\Omega, R_E = 1\text{k}\Omega, r_s = 100\text{k}\Omega, R_L = 4.7\text{k}\Omega, V_{CC} = 5\text{V}, \beta_0 = 100, V_{BEon} = 0.7\text{V}, V_A = \infty, C_{\mu} = 2\text{pF}, C_{\pi} = 10\text{pF}.$$

Find: \$C_M\$ & \$f_{3db}\$.

Soln. High-freq hybrid- π model: AC

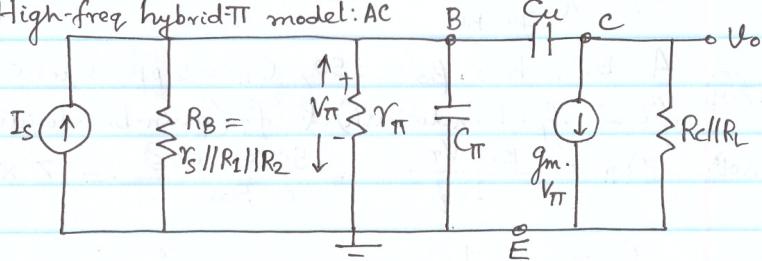

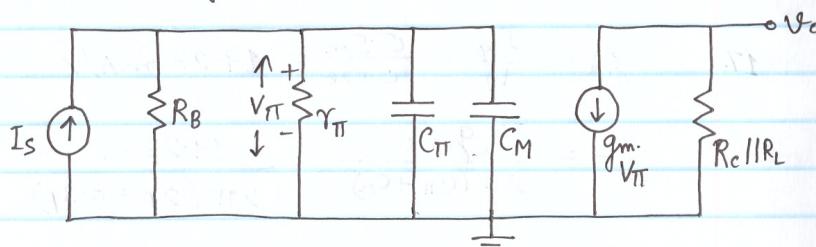(Note: \$R_E\$ & \$C_E\$ are shorted/ignored at high freq.)
Modified hybrid- π model with \$C_M\$ (Miller cap): AC



$$R_{TH} = R_1 || R_2 = 200\text{k} || 220\text{k} = 104.8\text{k}\Omega$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{220\text{k}}{200\text{k} + 220\text{k}} \cdot 5 = 2.619\text{V}$$

$$I_{Bq} = \frac{V_{TH} - V_{BEon}}{R_{TH} + (1+\beta) R_E}$$

Draw the high-freq hybrid- π ckt.

$$R_1 = 200\text{k}\Omega, R_2 = 220\text{k}\Omega, R_C = 2.2\text{k}\Omega, R_E = 1\text{k}\Omega, r_s = 100\text{k}\Omega, R_L = 4.7\text{k}\Omega, V_{CC} = 5\text{V}, \beta_0 = 100, V_{BEon} = 0.7\text{V}, V_A = \infty, C_{\mu} = 2\text{pF}, C_{\pi} = 10\text{pF}.$$

Find: \$C_M\$ & \$f_{3db}\$.

$$I_{Cq} = \beta \cdot I_{Bq} =$$

$$g_m = \frac{I_{Cq}}{V_T} =$$

$$r_{\pi} = \frac{\beta \cdot V_T}{I_{Cq}} =$$

$$C_M = C_{\mu} [1 + g_m (R_C || R_L)]$$


(Ans)

$$R_B = r_s || R_1 || R_2 =$$


$$f_{3db} = \frac{1}{2\pi(R_B || r_{\pi})(C_{\pi} + C_M)}$$

Ckt. BW
at high
freq. =


(Ans)

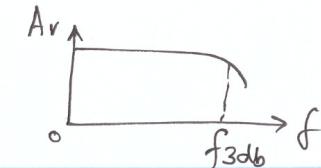

TYU6.7
(pg. 412)

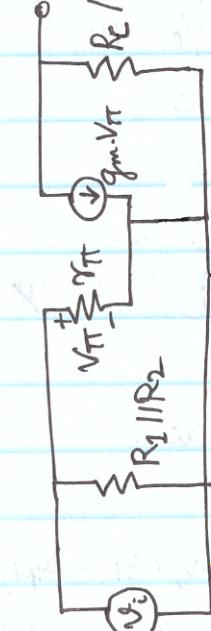

(Consider R_E is shorted through C_E)

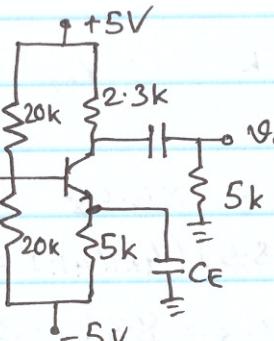

$\beta = 125, V_{BE(on)} = 0.7V, V_A = 200V, \text{ Find } R_o$

$$R_{TH} = R_1 // R_2 = 10k\Omega$$

$$I_{BQ} = \frac{0 - 0.7 - (-5)}{10 + (125 \times 5)} = 6.72 \mu A$$

$$I_{CQ} = 125 \times 6.72 \mu A = 0.84 mA$$

$$r_{\pi} = \frac{\beta \cdot V_T}{I_{CQ}} = \frac{125 \times 26 mV}{0.84 mA} = 3.87 k\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.84 m}{0.026} = 32.3 mA/V$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{200}{0.84 m} = 238 k\Omega$$


$$V_o = -g_m \cdot V_{\pi} (r_o // R_c // R_L) \quad \& \quad V_{\pi} = V_i$$

$$\therefore A_v = \frac{V_o}{V_i} = -g_m (r_o // R_c // R_L) = -(32.3)(238 k // 2.3 k // 5 k)$$

$$= -50.5 \quad (\text{Ans})$$

$$R_o = r_o // R_c = 238 k // 2.3 k = 2.28 k\Omega \quad (\text{Ans})$$

6.64
pg. 466

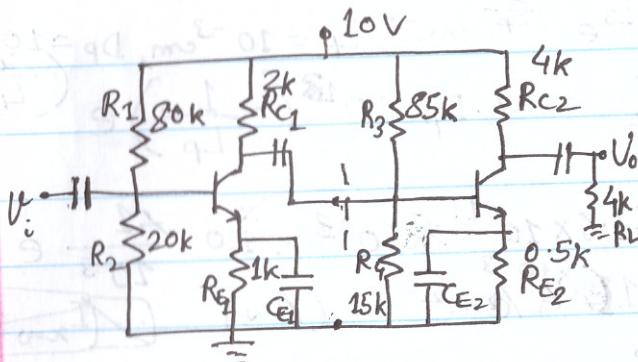

$\beta = 100$, $V_A = \infty$, Find Av.
while considering loading

$$V_{TH1} = \frac{(80k \parallel 20k)}{V_{cc}} = \frac{16k \times 10}{2V} = 2V$$

$$I_{B1} = \frac{2 - 0.7}{16 + (10k)(1k)} = 0.0111 \text{ mA}$$

$$I_{c1} = 100 \times 0.0111 \text{ mA} = 1.11 \text{ mA}$$

$$g_{m1} = \frac{I_{c1}}{V_T} = \frac{1.111 \text{ mA}}{26 \text{ m}} = 42.74 \text{ mA/V}$$

$$\gamma_{\pi_1} = \frac{\beta \cdot V_T}{I_{c1}} = \frac{100 \times 26 \text{ m}}{1.11 \text{ mA}} = 2.34 \text{ k}$$

$$\gamma_{o1} = \frac{V_A}{I_{c1}} = \frac{\infty}{1.11 \text{ mA}} = \infty$$

$$V_{TH2} = (85k \parallel 15k) \text{ } V_{cc} = 1.5V$$

$$R_{TH2} = R_3 \parallel R_4 = 12.75 \text{ k.}$$

$$I_{B2} = \frac{1.5 - 0.7}{12.75 \text{ k} + (10k)(0.5)} ; I_{c2} = 1.265 \text{ mA} ; g_{m2} = \frac{1.265 \text{ mA}}{0.026} = 48.65 \text{ mA/V}$$

$$\gamma_{\pi_2} = \frac{100 \times (0.026)}{1.265 \text{ mA}} = 2.06 \text{ k} ; \gamma_{o2} = \infty$$

$$Av_1 = -g_{m1} R_{c1} = -(42.7)(2) = -85.48$$

$$Av_2 = -g_{m2} (R_{c2} \parallel R_L) = -(48.5)(4k \parallel 4k) = -97.3$$

$$Av = Av_1 \cdot Av_2 = 85.48 \times 97.3 = 8317.204$$

$$R_{i2} = R_3 \parallel R_4 \parallel \gamma_{\pi_2} = 15k \parallel 85k \parallel 2.06k = 1.773k$$

$$Av'_1 = -g_{m1} (R_{c1} \parallel R_{i2}) = -(42.7)(2 \parallel 1.773k) = -40.18$$

$$\therefore Av' = Av'_1 \cdot Av_2 = 40.17 \times 97.3 = 3909$$

\therefore Loading of stage 2 reduces overall V-gain.