

Tutorial

1. Calculate intrinsic carrier concentration (conc.) of germanium at 30°C .

Solⁿ

$$n_i = B \cdot T^{\frac{3}{2}} \cdot e^{\left(\frac{-E_g}{2kT}\right)}$$

$$\begin{aligned} &= (1.66 \times 10^{15}) \times (30 + 273)^{1.5} \times e^{\frac{-0.66}{2 \times 86.17 \times 10^{-6} \times 303}} \\ &= (2.83 \times 10^{13}) \text{ per cm}^3 \quad (\text{Ans}) \end{aligned}$$

2. A Si block is at 300K, which is doped with Boron of conc. $5.6 \times 10^{18} \text{ cm}^{-3}$. Calculate the concentration of e^- & h^+ at thermal equilibrium.

Solⁿ

$$T = 300 \text{ K} ; N_a = 5.6 \times 10^{18} \text{ cm}^{-3}$$

$$n_i = B \cdot T^{\frac{3}{2}} \cdot e^{\frac{-E_g}{2kT}}$$

$$\begin{aligned} &= 5.23 \times 10^{15} \times 300^{1.5} \times e^{\frac{-1.1}{2 \times 86.17 \times 10^{-6} \times 300}} \\ &= 1.5 \times 10^{10} \text{ cm}^{-3} \end{aligned}$$

Now, B doping means tri-valent impurity addition, which further means p-type extrinsic material.

$$\therefore N_a \gg n_i$$

$$\therefore p_o \cong N_a = 5.6 \times 10^{18} \text{ cm}^{-3} \quad (\text{Ans})$$

We know,

$$n_o = \frac{n_i^2}{p_o} = \frac{n_i^2}{N_a} = \frac{(1.5 \times 10^{10})^2}{5.6 \times 10^{18}}$$

$$= 40.17 \text{ cm}^{-3} \quad (\text{Ans})$$

3. Consider a Si block at 300°K that has been doped with 'P' atoms. Assume, $\mu_n = 1380 \text{ cm}^2/\text{V-s}$, $\mu_p = 480 \text{ cm}^2/\text{V-s}$, $E = 220 \text{ V/cm}$, & $N_d = 9.1 \times 10^{16} \text{ cm}^{-3}$. Calculate drift current density.

Solⁿ. 'P' doping means pentavalent, which leads to n-type.
 $\therefore n \approx N_d = 9.1 \times 10^{16} \text{ cm}^{-3}$ (Majority conc.)
 $\& p = \frac{n_i^2}{n} = \frac{(1.5 \times 10^{10})^2}{9.1 \times 10^{16}} = 2.47 \times 10^3 \text{ cm}^{-3}$ (Minority conc.)

As, $N_d \gg p$, or $n \gg p$

Conductivity, $\sigma = q \cdot \mu_n \cdot n + q \cdot \mu_p \cdot p \approx q \cdot \mu_n \cdot n$
 $= (1.6 \times 10^{-19})(1380)(9.1 \times 10^{16})$
 $= 20.09 \text{ per Ohm-cm}$
 $= 20.09 / \Omega\text{-cm}$


We know,

drift current density: $J = \sigma \cdot E$
 $= (20.09)(220)$
 $= 4.42 \times 10^3 \text{ A/cm}^2$
 (Ans)

4. A block of Si has e^- concentration that linearly varies from $n = 10^{13} \text{ cm}^{-3}$ to 10^{18} cm^{-3} over a distance $x = 0.1$ to $4 \mu\text{m}$. If $T = 27^{\circ}\text{C}$ & diffusion co-efficient $D_n = 36 \text{ cm}^2/\text{s}$, calculate diffusion I-density:

Solⁿ We know, $J_n = q \cdot D_n \cdot \frac{dn}{dx} = q \cdot D_n \cdot \frac{\Delta n}{\Delta x}$
 $= (1.6 \times 10^{-19})(36) \left(\frac{10^{18} - 10^{13}}{4 \times 10^{-4} - 0.1 \times 10^{-4}} \right)$
 $= 14.76 \times 10^3 \text{ A/cm}^2$ (Ans)

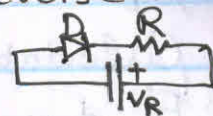5. Calculate V_{bi} & C_j of a Ge p-n junction diode at 30°C . Assume, $N_a = 10^{17} \text{ cm}^{-3}$, $N_d = 10^{15} \text{ cm}^{-3}$, $C_{j0} = 0.5 \text{ pF}$, reverse biased voltage $V_R = 1.1 \text{ V}$ & 4.5 V .



Solⁿ We know, $n_i = B \cdot T^{3/2} \cdot e^{\frac{-E_g}{2kT}}$
 @ 30°C for Ge, $n_i = 2.83 \times 10^{13} \text{ cm}^{-3}$

We know, $V_T \approx 26 \text{ mV @ } 300 \text{ K}$

$$V_{bi} = \left(\frac{kT}{q} \right) \ln \left[\frac{N_a N_d}{n_i^2} \right]$$

$$= \left[\frac{1.38 \times 10^{-23} \times 303}{1.6 \times 10^{-19}} \right] \ln \left[\frac{10^{17} \cdot 10^{15}}{(2.83 \times 10^{13})^2} \right]$$

$$= 0.306 \text{ V} \quad (\text{Ans})$$

We know,

$$C_j = C_{j0} \left(1 + \frac{V_R}{V_{bi}} \right)^{-\frac{1}{2}}$$

$$= (0.5 \times 10^{-12}) \left(1 + \frac{1.1}{0.306} \right)^{-\frac{1}{2}}$$

$$= 233.25 \text{ fF} \quad [\text{@ } V_R = 1.1 \text{ V}] \quad (\text{Ans})$$

$$\text{Also, } C_j = (0.5 \times 10^{-12}) \left(1 + \frac{4.5}{0.306} \right)^{-\frac{1}{2}}$$

$$= 126.16 \text{ fF} \quad [\text{@ } V_R = 4.5 \text{ V}]$$

6. Consider all the given & calculated parameters in the previous problem. Calculate time constants if a high pass filter_{like ckt} is realized by using a $10 \text{ M}\Omega$ resistor and the diode.


Solⁿ. $\tau = R.C_j$

$$\tau_1 = 10 \times 10^6 \times 233.25 \times 10^{-15}$$

$$= 2.33 \mu s \quad (\text{Ans})$$

$$\tau_2 = 10 \times 10^6 \times 126.16 \times 10^{-15}$$

$$= 1.26 \mu s \quad (\text{Ans})$$

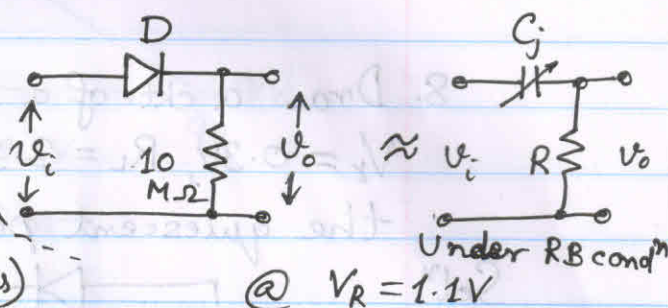

@ $V_R = 1.1V$

@ $V_R = 4.5V$

7. Calculate diode voltages while current flowing through it is $+4.2 \text{ mA}$ & $+1.2 \times 10^{-14} \text{ A}$. Assume, $T = 300 \text{ K}$, $I_s = 10^{-14} \text{ A}$, $n = 1$. Find the material of the diode.

Solⁿ. We know, $i_D = I_s \left[e^{\frac{V_D}{nV_T}} - 1 \right]$

$$\Rightarrow e^{\frac{V_D}{V_T}} = \frac{i_D}{I_s} + 1$$

$$\Rightarrow \frac{V_D}{V_T} = \ln \left[\frac{i_D}{I_s} + 1 \right]$$

$$\Rightarrow V_D = V_T \cdot \ln \left[\frac{i_D}{I_s} + 1 \right]$$

At, $i_D = 4.2 \text{ mA}$,

$$V_D = (26 \text{ mV}) \ln \left(\frac{4.2 \text{ mA}}{10^{-14}} + 1 \right) = 0.6958 \text{ V}$$



At, $i_D = +1.2 \times 10^{-14} \text{ A}$,

$$V_D = (26 \times 10^{-3}) \ln \left[\frac{+1.2 \times 10^{-14}}{10^{-14}} + 1 \right] = +0.0204 \text{ V}$$

Since, $V_D \approx 0.7 \text{ V}$, the diode is made of Si.

8. Draw a ckt. of a simple half wave rectifier. Let, $V_f = 0.3V$, $R_L = 3.3k\Omega$, $v_i(AC) = 9V \sin \omega t$, $r_f = 5\Omega$. Find the quiescent point at $v_i = +V_M$ & P_D .

Solⁿ.

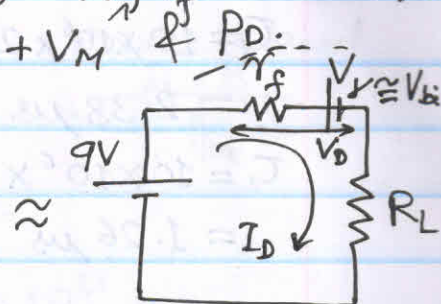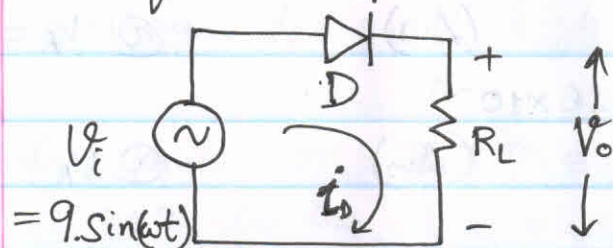

Assume, $f = 50Hz$

(During forward bias)
 $v_i = V_M$

By applying KVL in the above ckt., (@ $v_i = +V_M$)

$$I_D = \frac{V_M - V_f}{R_L + r_f} = \frac{9 - 0.3}{3.3 \times 10^3 + 5} = 2.63 \text{ mA} \quad (\text{Ans})$$

Also,

$$V_D = V_f + I_D \cdot r_f = 0.3 + (2.63 \text{ mA}) \times 5 = 313.15 \text{ mV} \quad (\text{Ans})$$

$$\begin{aligned} \text{We know, } P_D &= V_D \cdot I_D = (2.63 \text{ mA})(313.15 \text{ mV}) \\ &= 823.58 \mu\text{W} \quad (\text{Ans}) \end{aligned}$$

9. Find the DC load line for the above problem.

Solⁿ. Load line intersects the V-I characteristics:

$$\text{@ } v_i = +V_M; \quad x\text{-axis: } V_{F_{\max}} = V_M = 9V$$


$$y\text{-axis: } I_y = \frac{V_{F_{\max}}}{R_L + r_f} = \frac{9}{3.3k + 5} = 2.72 \text{ mA}$$

$$\text{@ } v_i = -V_M; \quad x\text{-axis: } V_{F_{\min}} = -V_M = -9V = V_R = V_D$$

$$y\text{-axis: } I_y = i_D = I_s \left[e^{\frac{V_D}{nV_T}} - 1 \right]$$

Assume, $I_s = 10^{-14} \text{ A}$.
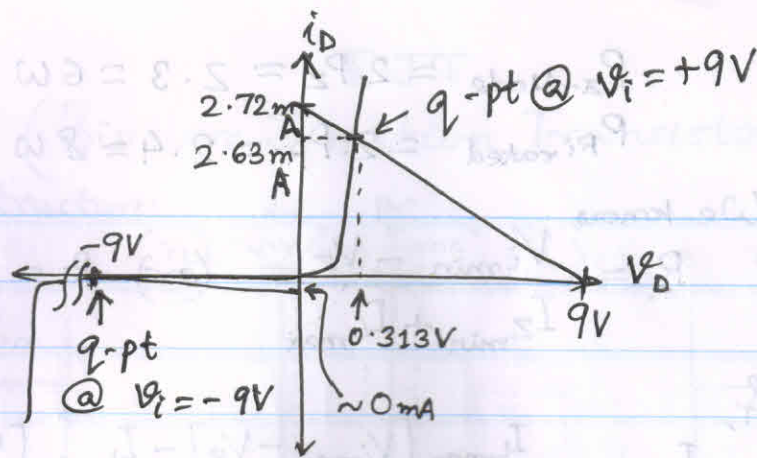
$$\Rightarrow I_y = 10^{-14} \left[e^{\frac{-9}{1 \times 26 \text{ mV}}} - 1 \right] = 0 \text{ mA}$$



10. A full-wave rectifier is operated at a 50Hz AC with an input of $12 \sin \omega t$. If a load resistance is $2.2k\Omega$ & allowed ripple voltage is $0.5V$, calculate the value of a filter capacitor.

Solⁿ. $V_M = 12V$, $f = 50Hz$, $V_r = 0.5V$, $R_L = 2.2k\Omega$, $V_f = 0.7V$
 Assume S_i , $r_f \approx 0$
 We know,


$$C_{\text{filter}} = \frac{V_M - V_r}{2f \cdot R_L \cdot V_r}$$

$$= \frac{12 - 0.7}{2 \times 50 \times 2.2 \times 10^3 \times 0.5} = 102 \mu F \quad (\text{Ans})$$

Now, voltage rating of C_{filter} is: $\geq 2 \cdot V_M$
 $= 25V \quad (\text{Ans})$

11. Draw a zener voltage regulator. Assume, $V_i = 10$ to $14V$, $I_L = 0$ to $200mA$, $V_L = 6V$. Design the ckt.

Solⁿ.

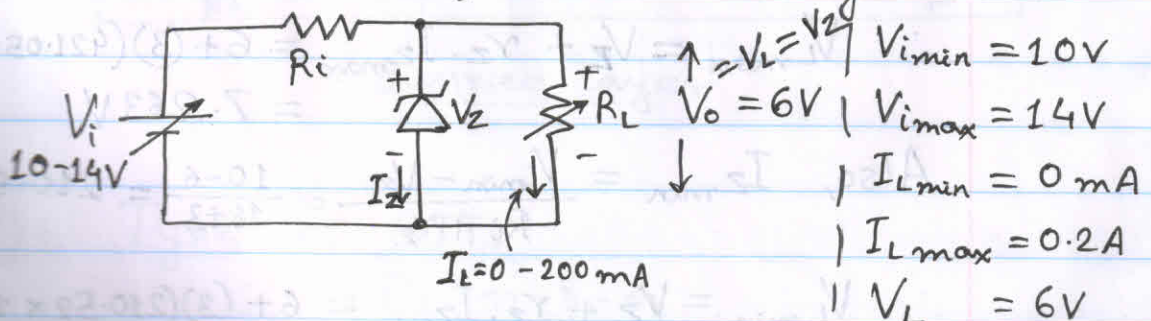

We know, $V_Z = V_L = 6V$

$$I_{Z\max} = \frac{V_{i\max} - V_Z}{R_i} - I_{L\min}$$

$$\left. \begin{aligned} P_{Z\text{-diode}} &= 2 \cdot P_Z = 2 \cdot 3 = 6 \text{ W} \\ P_{R_i \text{ rated}} &= 2 \cdot P_{R_i} = 2 \cdot 4 = 8 \text{ W} \end{aligned} \right\} (\text{Ans})$$

We know,

$$R_i = \frac{V_{i\min} - V_Z}{I_{Z\min} + I_{L\max}} \quad (\text{or}) \quad R_i = \frac{V_{i\max} - V_Z}{I_{Z\max} + I_{L\min}}$$

&

$$I_{Z\max} = \frac{I_{L\max} [V_{i\max} - V_Z] - I_{L\min} [V_{i\min} - V_Z]}{V_{i\min} - 0.9V_Z - 0.1V_{i\max}}$$

$$\Rightarrow I_{Z\max} = \frac{0.2[14-6] - 0[10-6]}{10 - (0.9)(6) - (0.1)(14)} = 0.5 \text{ A} \quad (\text{Ans})$$

$$\therefore R_i = \frac{14-6}{0.5+0} = 16 \, \Omega \quad (\text{Ans})$$

Max. Power loss across R_i is:

$$P_{R_i} = \frac{(V_{i\max} - V_Z)^2}{R_i} = \frac{(14-6)^2}{16} = 4 \text{ W} \quad (\text{Ans})$$

$$\text{Now, } I_{Z\min} = \frac{V_{i\min} - V_Z}{R_i} = \frac{10-6}{16} = 0.25 \text{ A} \quad (\text{Ans})$$

$$P_Z = V_Z \cdot I_{Z\max} = 6 \cdot 0.5 = 3 \text{ W} \quad (\text{Ans})$$

12. Calculate line & load regulation, if $r_Z = 3 \, \Omega$

$$\text{Sol}^n. \text{ We know, } I_{Z\max} = \frac{V_{i\max} - V_Z}{R_i + r_Z} = \frac{14-6}{16+3} = 421.05 \text{ mA}$$

$$\therefore V_{L\max} = V_Z + r_Z \cdot I_{Z\max} = 6 + (3)(421.05 \times 10^{-3}) = 7.263 \text{ V}$$

$$\text{Also, } I_{Z\min} = \frac{V_{i\min} - V_Z}{R_i + r_Z} = \frac{10-6}{16+3} = 210.52 \text{ mA}$$

$$\therefore V_{L\min} = V_Z + r_Z \cdot I_{Z\min} = 6 + (3)(210.52 \times 10^{-3}) = 6.631 \text{ V}$$

$$V_o = 6.631 \text{ to } 7.263 \text{ V} \\ @ 10 \text{ V} \quad @ 14 \text{ V } V_i$$

$$I_L = 0 \text{ to } 200 \text{ mA}$$

$$7.263 \text{ V} \quad 6.663 \text{ V} @ V_0$$

12. We know, line regulation or source regulation:
(cont.) % line reg. = $\frac{\Delta V_L}{\Delta V_{i_{DC}}} \times 100$

$$= \frac{7.263 - 6.631}{14 - 10} = 15.8\% \quad (\text{Ans})$$

Consider, the effect of change in I_L at $V_i = 14 \text{ V}$:

$$\text{For, } I_L = 0 \text{ mA: } I_Z = \frac{14 - 6}{16 + 3} = 421.05 \text{ mA}$$

$$\therefore V_{L_{\text{no-load}}} = V_Z + r_Z \cdot I_Z = 6 + (3)(421.05 \text{ m}) = 7.263 \text{ V}$$

$$\text{For, } I_L = 200 \text{ mA: } I_Z = \frac{V_{i_{\text{max}}} - [V_Z + I_Z \cdot r_Z]}{R_i} - I_{L_{\text{max}}}$$

$$= \frac{14 - [6 + (3)(421)]}{16} - 0.2$$

$$= 221.06 \text{ mA}$$

$$\therefore V_{L_{\text{Full-load}}} = V_Z + r_Z I_Z = 6 + (3)(221) = 6.663 \text{ V}$$


We know,

$$\% \text{ load reg.} = \frac{V_{L_{\text{no-load}}} - V_{L_{\text{full-load}}}}{V_{L_{\text{full-load}}}} \times 100$$

$$= \frac{7.263 - 6.663}{6.663} \times 100$$

$$= 9.004\% \quad (\text{Ans})$$

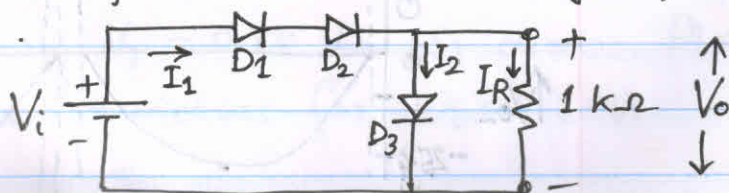13. Consider the ckt. and find the input voltage, if $V_0 = 0.6 \text{ V}$ and $I_S = 2 \times 10^{-13} \text{ A}$.



Solⁿ. $I_2 = I_S \cdot e^{\left(\frac{V_0}{V_T}\right)} = 2 \times 10^{-13} \cdot e^{\left(\frac{0.6}{0.026}\right)} = 2.105 \text{ mA}$


$I_R = \frac{V_0}{R} = \frac{0.6}{1k} = 0.6 \text{ mA}$

$I_1 = I_2 + I_R = 2.105 \text{ mA} + 0.6 \text{ mA} = 2.705 \text{ mA}$


$V_D = V_T \cdot \ln\left(\frac{I_1}{I_S}\right) = 26 \times 10^{-3} \cdot \ln\left(\frac{2.705 \times 10^{-3}}{2 \times 10^{-13}}\right)$
 $= 0.6065 \text{ V}$

$V_i = 2 \cdot V_D + V_0 = 2(0.6065) + 0.6 = 1.81 \text{ V} \quad (\text{Ans})$

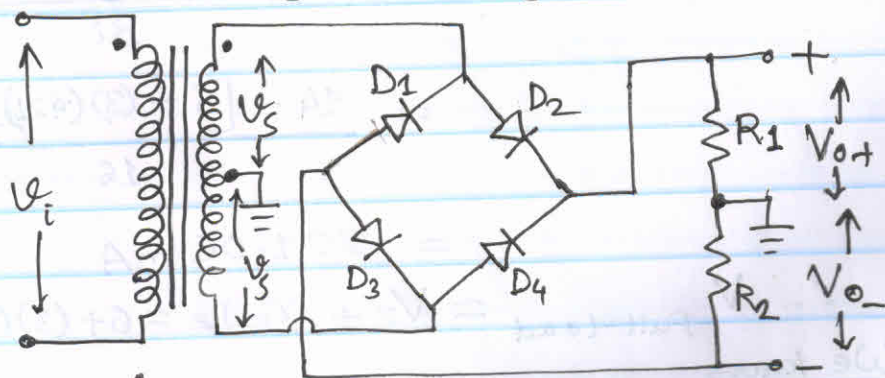
14. Draw the output waveforms of the following ckt:
 $V_s = 26 \cdot \sin(2\pi 60t)$




Solⁿ.

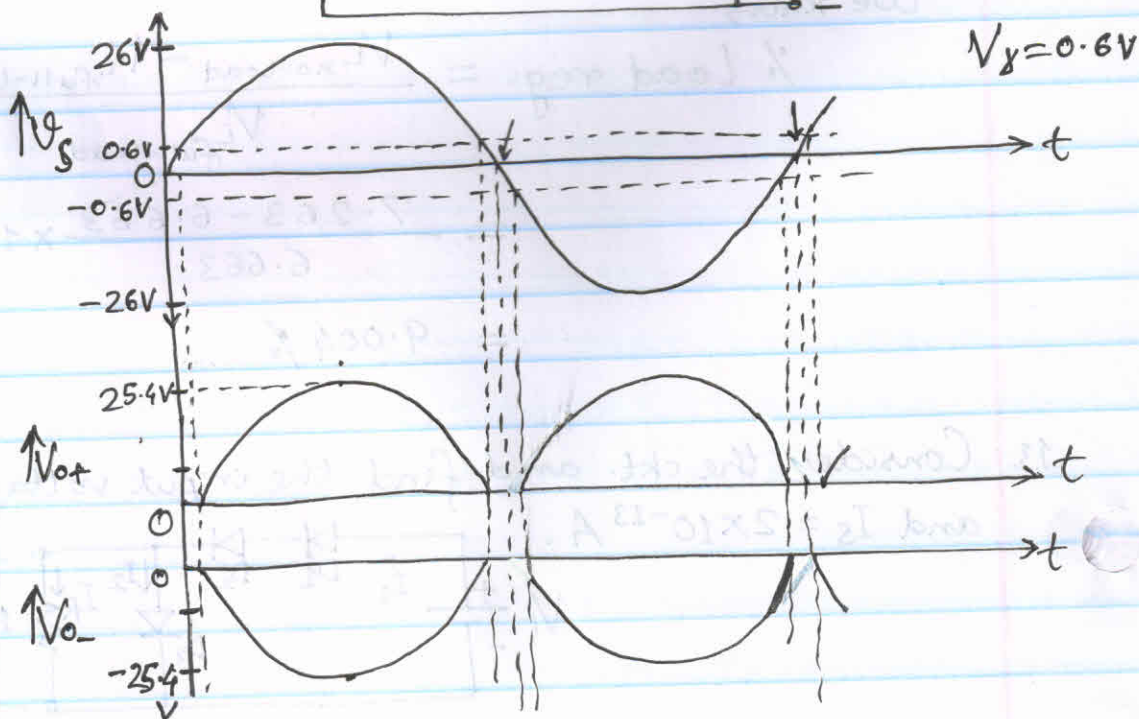

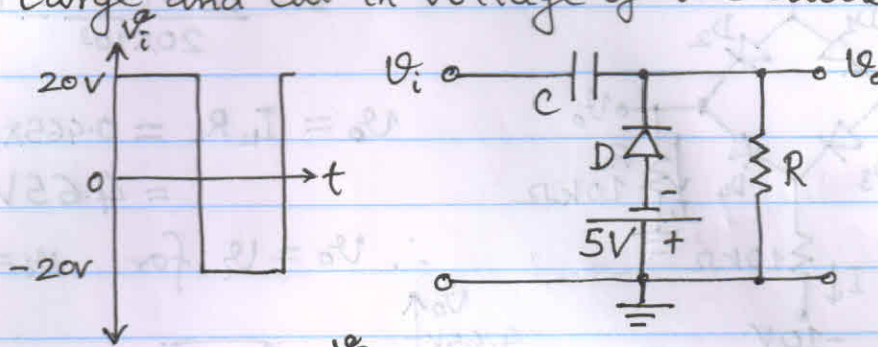15. Draw the ^{steady-state} output waveform if RC time constant is large and cut-in voltage of the diode is 0V.




Solⁿ.

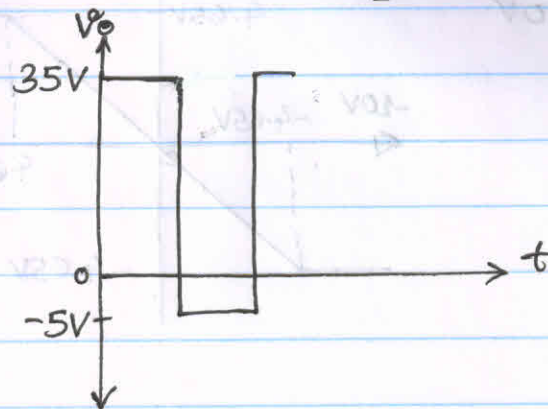

Steps ?

16. Draw the ckt. of a bipolar regulated linear power supply by using a center-tapped transformer and a bridge rectifier.

Solⁿ.

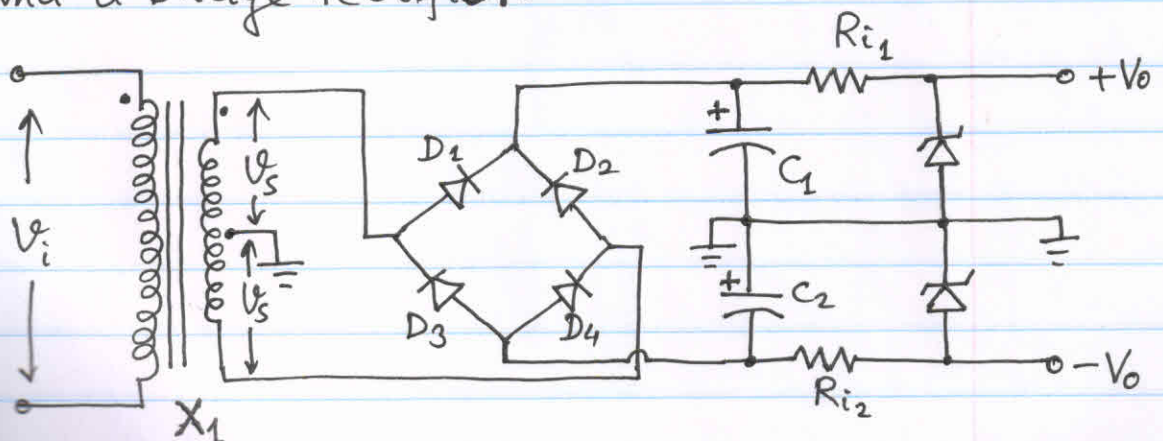

17. For the ckt. shown, $V_f = 0.7V$ for Si diodes. Plot the transfer characteristics for $V_i = \pm 10V$.