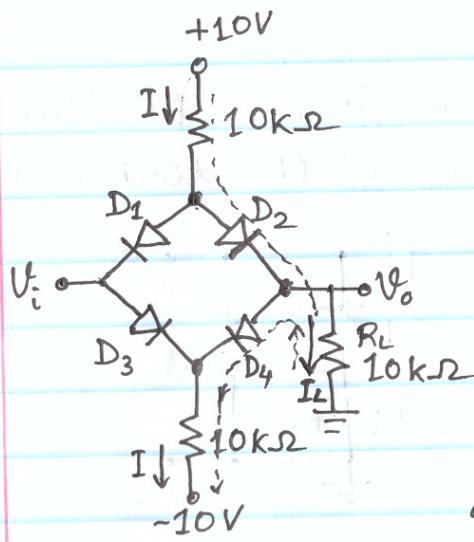


Sol<sup>n</sup>:




For,  $V_i > 0$ ,  $D_1$  &  $D_4$  are off.

$$I_L = \frac{10 - 0.7}{20 \times 10^3} = 0.465 \text{ mA}$$

$$V_o = I_L R_L = 0.465 \times 10^3 \times 10 \times 10^3 = 4.65 \text{ V}$$

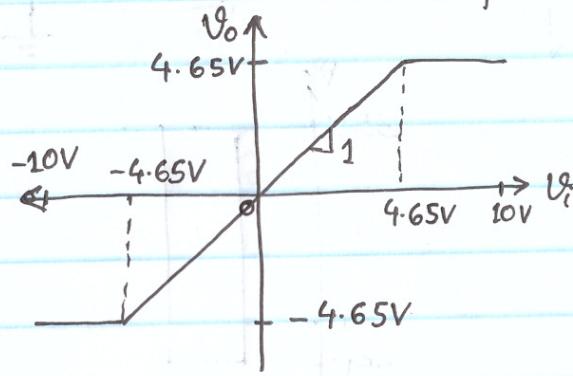$\therefore V_o = V_i$  for  $V_i = \pm 4.65 \text{ V}$




Similarly, while  $V_i < 0$ ,  $D_2$  &  $D_3$  are off.

$$-I_L = \frac{10 - 0.7}{20 \times 10^3} = 0.465 \text{ mA}$$

$$\&, -V_o = -I_L \cdot R_L = -4.65 \text{ V}$$

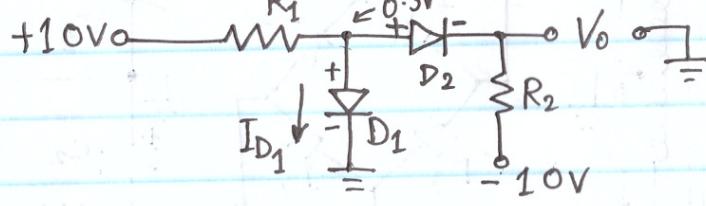18. Find  $I_{D_1}$  &  $V_o$  if  $V_g = 0.3 \text{ V}$ ,  $R_1 = 6.8 \text{ k}\Omega$  &  $R_2 = 12 \text{ k}\Omega$




Sol<sup>n</sup>: While,  $D_1$  &  $D_2$  are ON,  $V_o = +3 - 3 = 0 \text{ V}$  (Ans)

$$\text{Now, } I_{D_1} = \frac{10 - 0.3}{6.8 \times 10^3} = \frac{0 - (-10)}{12 \times 10^3} = 0.593 \text{ mA}$$

(Ans)

19.

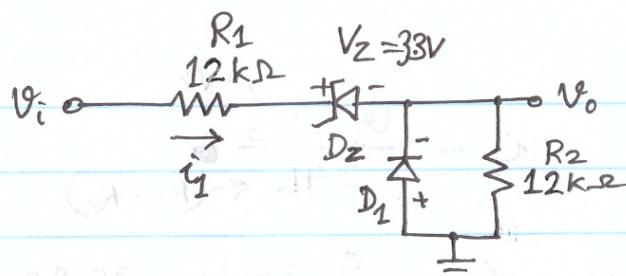

$$V_y = 0$$

$$V_i = -20V \text{ to } +20V$$

Plot:  $V_o$  Vs  $V_i$  ( $i_1$  Vs  $V_i$ )

Sol<sup>n</sup>. During,  $V_i = 0 \text{ to } -20V$ , zener & normal D are conducting  $\Rightarrow V_o$  ( $20V \text{ to } 0V$ ) = 0

For,  $V_i = 0 \text{ to } +3.3V$ , zener is in reverse blocking mode (not in breakdown)  $\Rightarrow i_1 = 0 \text{ & } V_o = 0$

For,  $V_i > 3.3V$ , Z-diode enters into brk-down state.


$$i_1 = \frac{V_i - 3.3}{12k + 12k} \quad A$$

$$\&, \quad V_o_{(3.3 \text{ to } 20V)} = \left[ \frac{V_i - 3.3}{12k + 12k} \right] (12k) = \frac{V_i - 3.3}{2}$$

At,  $V_i = +20V$ ,

$$i_1 = \frac{20 - 3.3}{24k} = 695.83 \mu A$$


$$V_o_{(20V)} = 8.35V$$

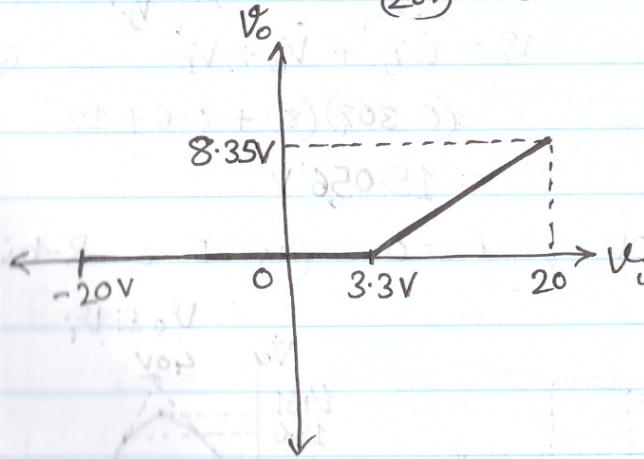


For,  $V_i < 0$ ,  $V_o = 0V$  &  $-i_1 = \frac{0 - V_i}{12k} = \frac{0 - (-20)}{12k}$   
 $R_1 \quad i_1 = -1.666 \text{ mA}$

$$\text{For, } V_i > 3.3V, \quad i_1 = \frac{V_i - 3.3}{24k} \leftarrow \frac{V_i - 3.3}{R_1 + R_2}$$
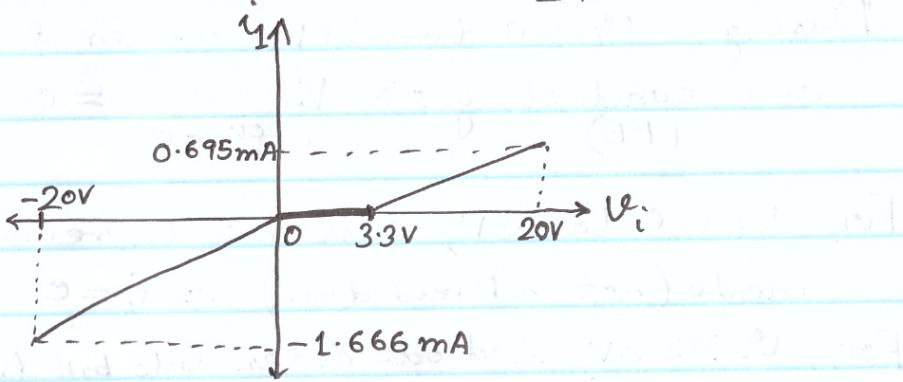
$$\text{At, } V_i = +20V, \quad i_1 = \frac{20 - 3.3}{24k} = 695.83\mu A$$




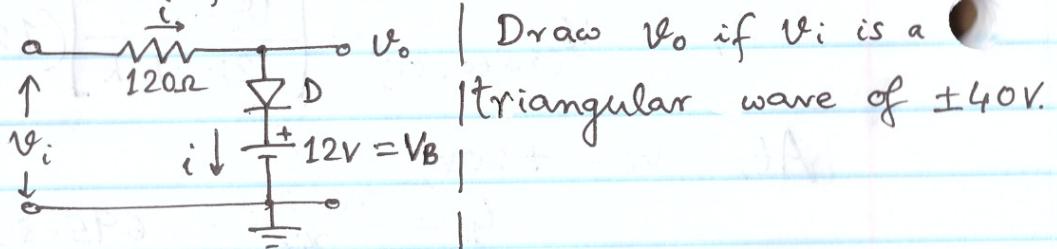
20. If  $V_g = 0.6V$ ,  $r_f = 8\Omega$ ,  $V_i = \pm 40V$ , plot  $V_o$  Vs.  $V_i$ .



$$\text{Soln. For, } V_i = +40V, \quad i = \frac{40 - 0.6 - 12}{120 + 8} = 214.06 \text{ mA}$$

$$\begin{aligned} V_o &= i \cdot r_f + V_B + V_D \\ &= (0.214)(8) + 0.6 + 12 \\ &= 14.31V \end{aligned}$$

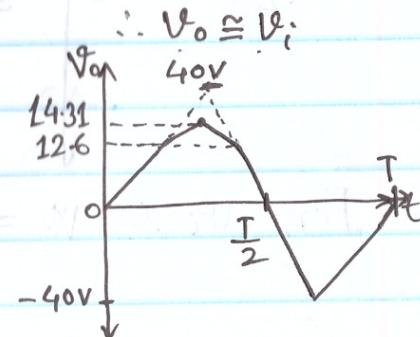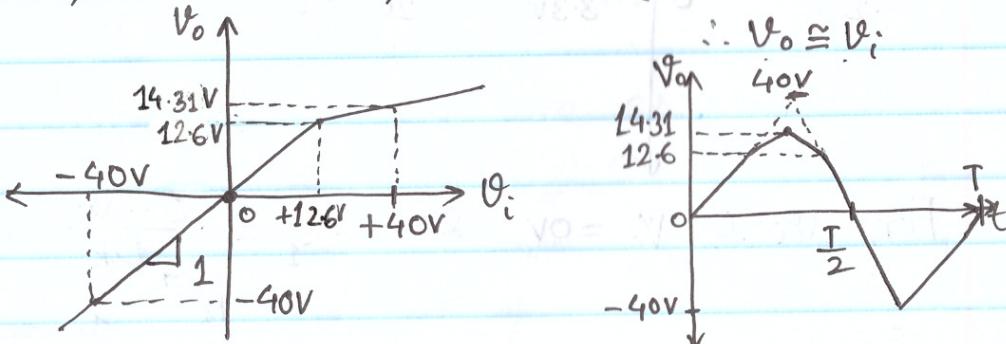
For,  $V_i = -40V$ ,  $i = 0$  (as D is R-biased)




## BJT

**(Bipolar Junction Transistors)**

i) Basic Structure:

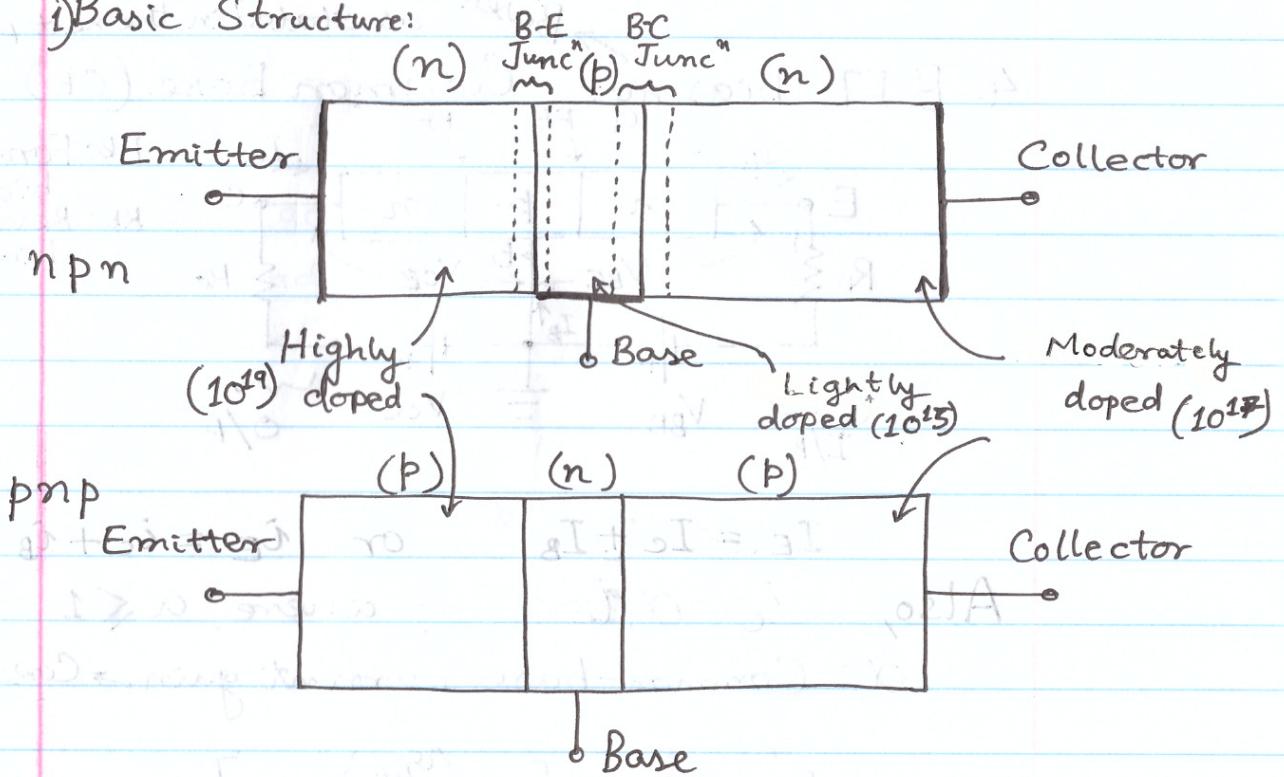

2) Cross-section: npn BJT

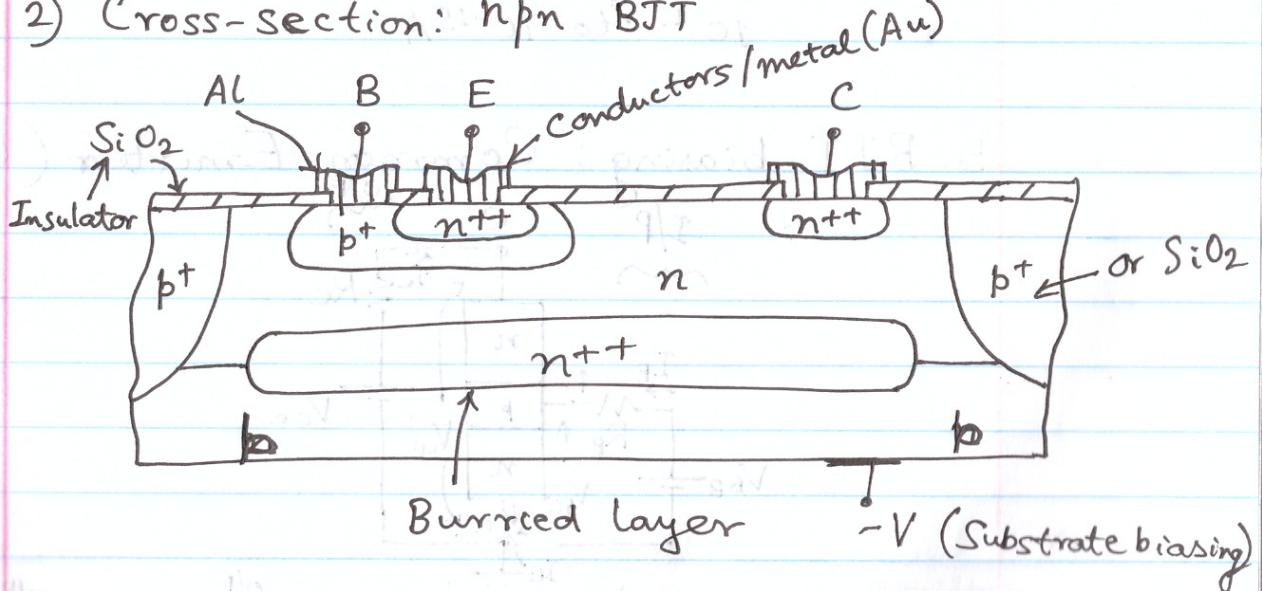


3) Types of BJTs:

- 1) n-p-n
- 2) p-n-p

Based on modes of operation,  
as stated in the next page.

#### 4. BJT biasing: Common Base (CB)

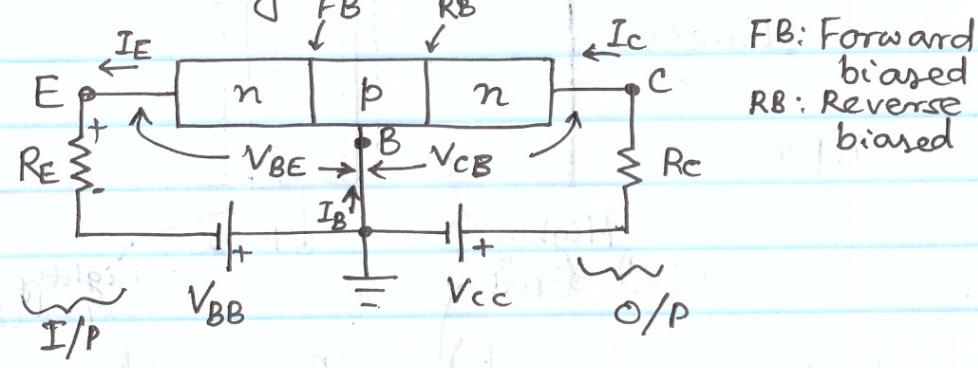

$$I_C = \alpha \cdot I_E$$


$$i_C = \alpha \cdot i_E \quad ; \text{ where, } \alpha \ll 1$$

$\alpha$ : Common-base current gain  $\rightarrow$  Constant no.

$$i_E = I_{EO} \left[ e^{\left( \frac{V_{BE}}{V_T} \right)} - 1 \right]$$

$10^{-12}$  to  $10^{-15} A$

#### 5. BJT biasing: Common Emitter (CE)

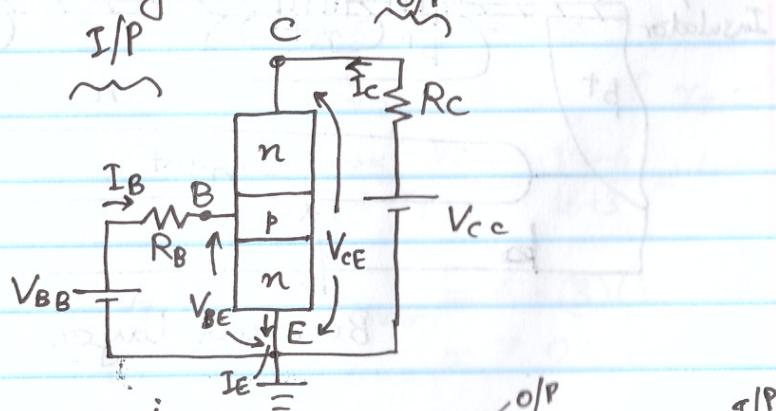

$$i_E = i_C + i_B \quad ; \quad i_C = \beta \cdot I_B$$

$$\Rightarrow i_E = (1 + \beta) i_B$$

$\beta$ : Common emitter


current gain.

$$\therefore i_C = \frac{\beta}{1 + \beta} i_E$$

$$\alpha = \frac{\beta}{1+\beta}$$



$$(f) \quad \beta = \frac{\alpha}{1-\alpha}$$

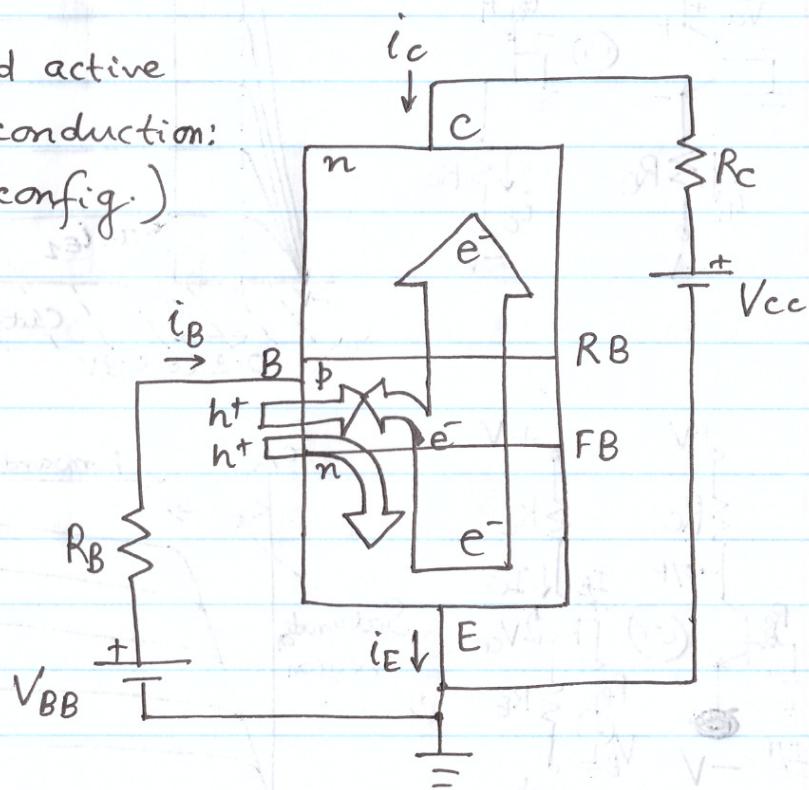5. Forward active mode conduction:  
(CE config.)



$$V_{CC} > V_{BB}$$

6. BJT symbols:

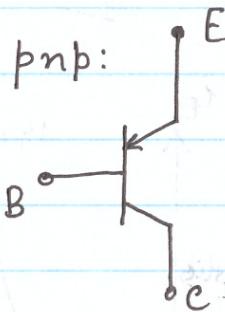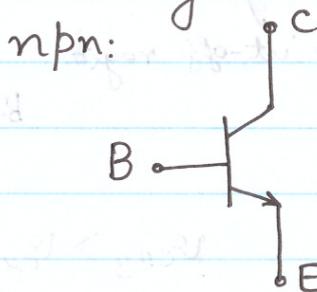

7. a. Transistor modes of operation: (BJT)






- 1) Common base (CB)
- 2) Common emitter (CE)
- 3) Common collector (CC)

b. Transistor (BJT) regions of operation:


- 1) Cut-off (OFF switch)
- 2) Saturation (resistor-like)
- 3) Active - Forward (ON switch)  
Reverse with resistance  
(special resistor)
- 4) Breakdown (causes permanent damage)

7c.



V-I characteristics:

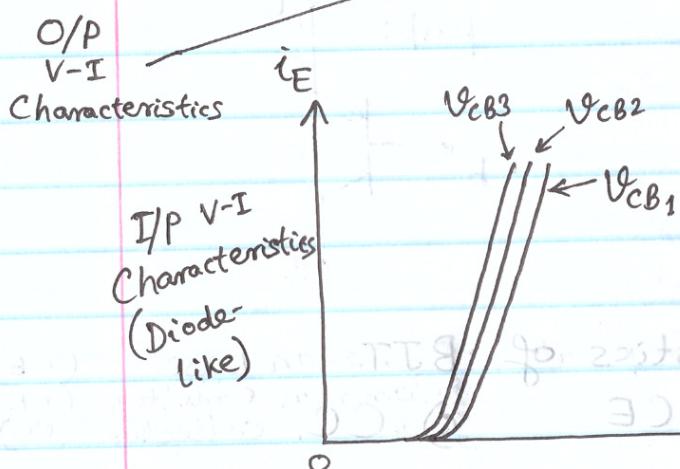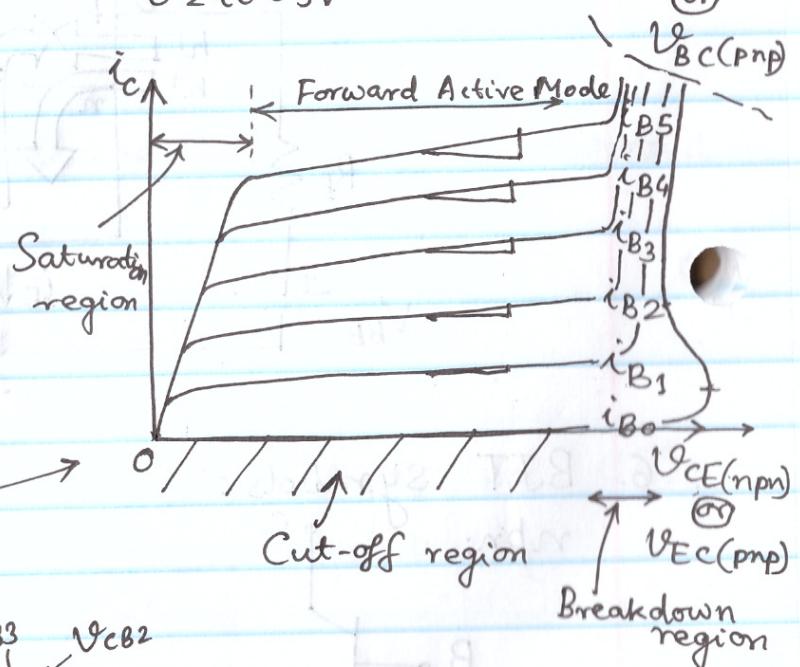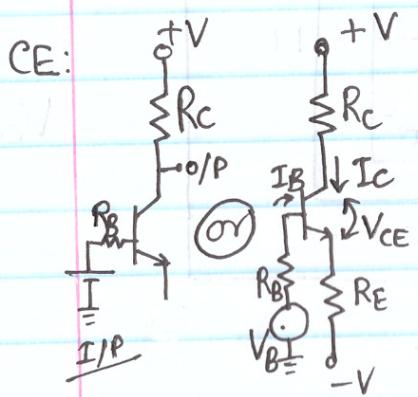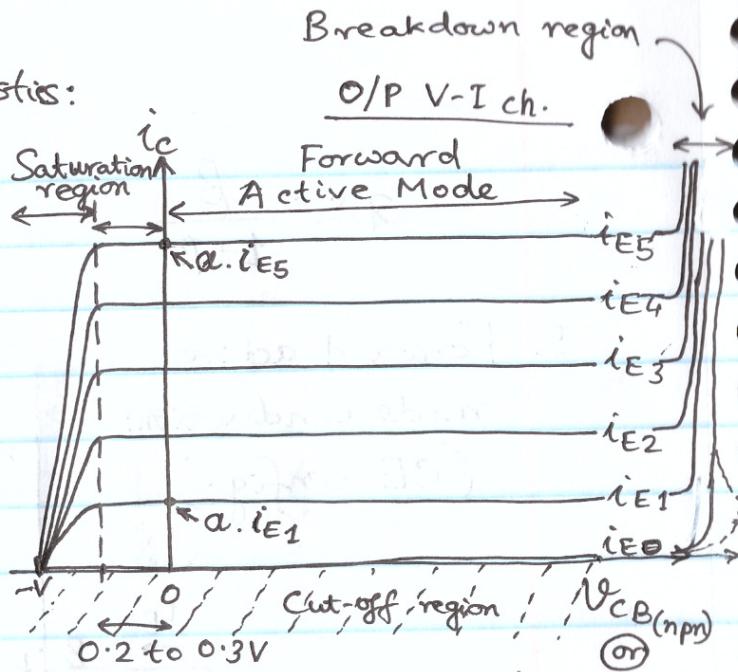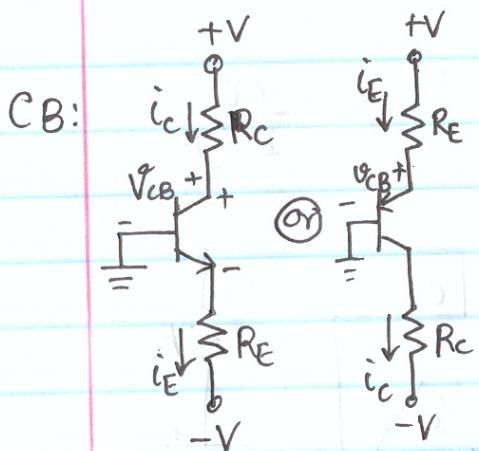


$$V_{CB3} > V_{CB2} > V_{CB1}$$

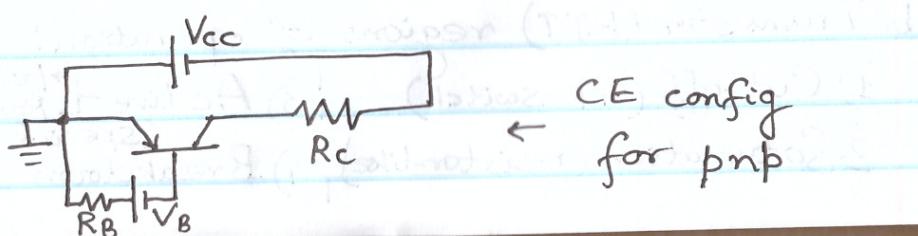

## BJT (cont.)

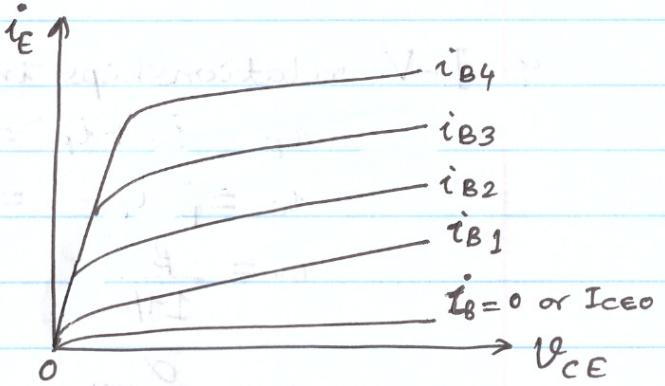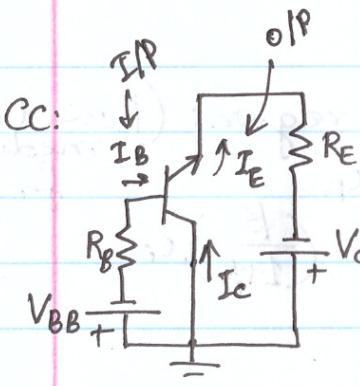

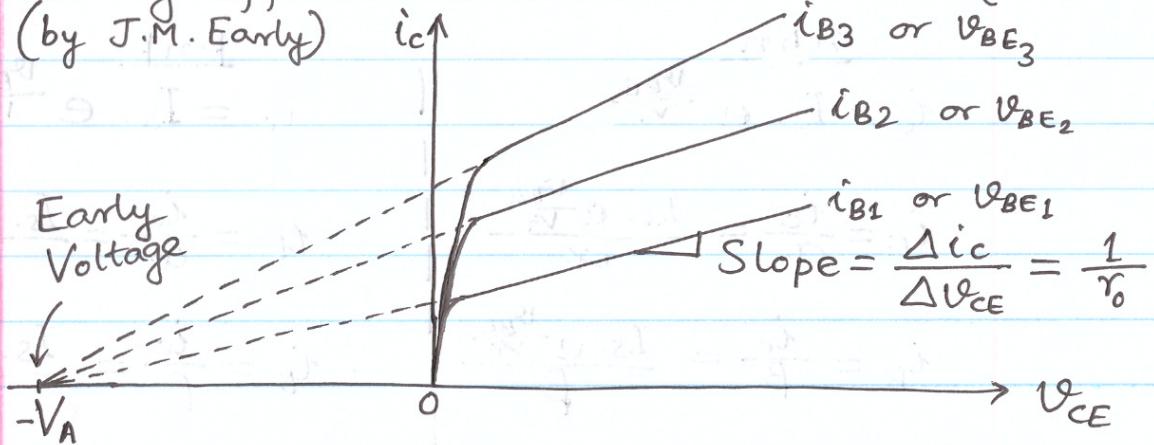8. Early effect & base width modulation (CE):  
(by J.M. Early)  $i_c \uparrow$



$R_0$ : O/P resistance

$$R_0 \approx \frac{V_A}{I_C}$$

$$i_C = I_s \cdot e^{\left(\frac{V_{BE}}{V_T}\right)} \cdot \left(1 + \frac{V_{CE}}{V_A}\right)$$

While early effect is considered.

$|V_A|$ : 50 to 300V (typically)

Base width modulation:  $V_{BE} \uparrow \quad i_B \uparrow \quad$  Junc<sup>n</sup> width (CB)  
Width of base region  $\uparrow \quad i_C \uparrow$