

Q1

If we want to use BJT as an amplifier, what biasing condition need to be applied across base-emitter and base-collector junctions?

Q2


If we want to use BJT as a switch, what should be regions of operations?

Q3

Most of the carriers flowing through the base of a BJT are majority carriers or minority carriers?

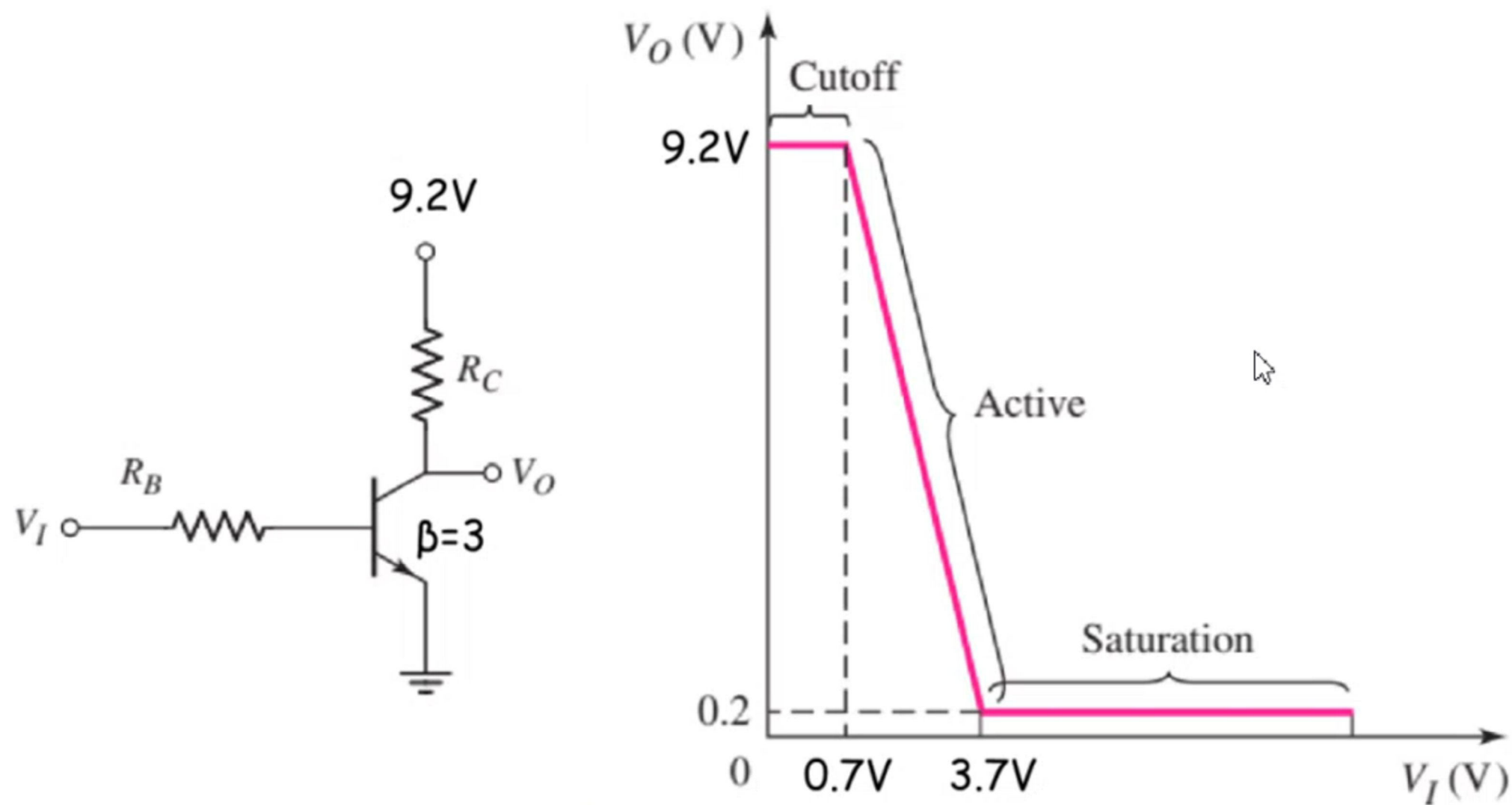**Q4**

What is the approximate gain of the amplifier shown in the Fig. below. The slope of the  $V_O - V_I$  graph in the active region is equal to  $-3$



## Q5

In the transfer characteristics of a MOSFET, the threshold voltage is the measure of the

- (a) minimum voltage to induce a n-channel/p-channel for conduction
- (b) minimum voltage till which temperature is constant
- (c) minimum voltage to turn off the device
- (d) none of the above mentioned is true

Q6

For the MOS capacitor with a n-type substrate, a \_\_\_\_\_ gate voltage must be applied to create the hole inversion layer.


- (a) zero
- (b) positive
- (c) negative
- (d) either positive or negative

**Q7**

What are the important characteristics of an ideal op-amp?

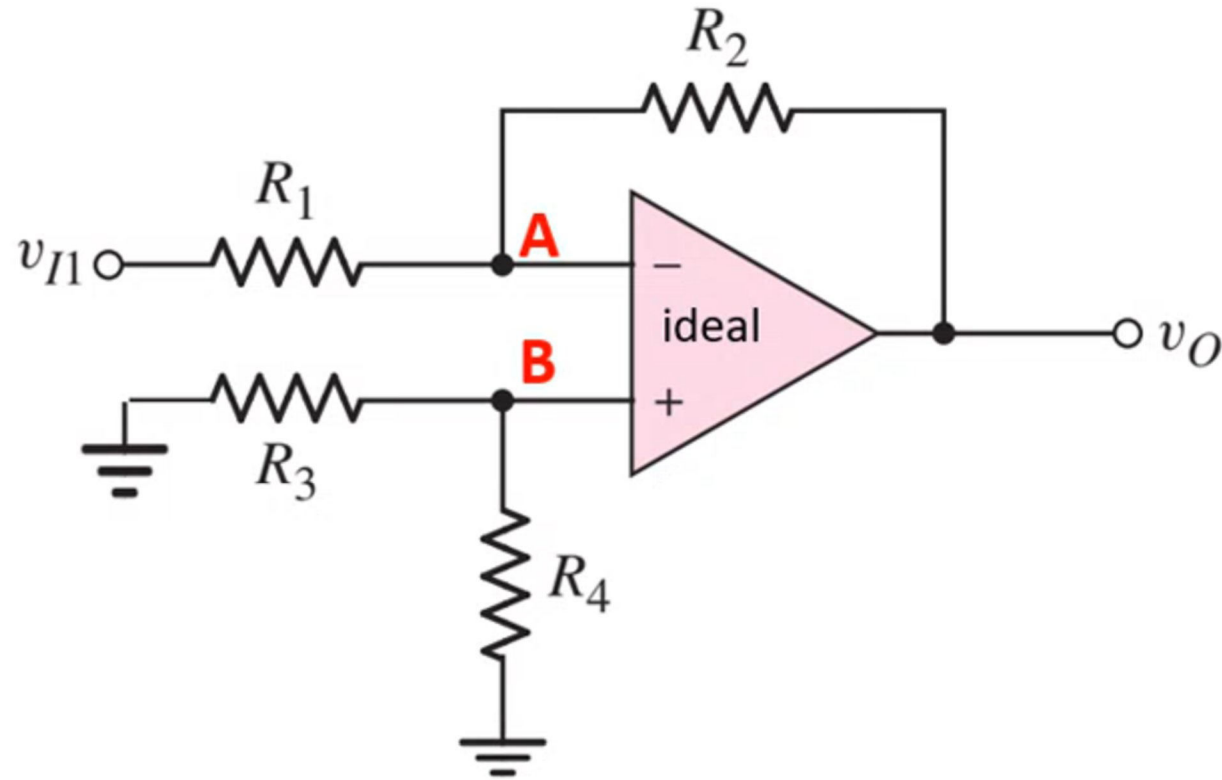Q8

What is the voltage at node A in the following op-amp circuit?





Q1

If for a BJT, the common base current gain is 0.98, then what is the value of its common emitter current gain?



Q2

Why do we use an emitter resistance in a common emitter biasing configuration?

### Q3

The BJT small signal output impedance  $r_o$  accounts for

- (a) change in  $i_c$  with  $v_{CE}$  in the active regime
- (b) change in  $i_c$  with  $v_{CE}$  in the saturation regime
- (c) change in  $i_b$  with  $v_{BE}$  in the active regime
- (d) change in  $i_b$  with  $v_{BE}$  in the saturation regime

Q4

In a BJT biased in common emitter configuration,  $V_{CEQ}$  depends on

- (a) collector resistance  $R_C$
- (b) emitter resistance  $R_E$
- (c) DC base current  $I_{BEQ}$
- (d) all of the above

**Q5**

Which is the correct statement among the following?

- (a) MOSFET is an uncontrolled device
- (b) MOSFET is a voltage controlled device
- (c) MOSFET is a current controlled device
- (d) MOSFET is a temperature controlled device

## Q6

The output characteristics of a MOSFET is a plot of


- (a)  $I_d$  as a function of  $V_{gs}$  with  $V_{ds}$  as a parameter
- (b)  $I_d$  as a function of  $V_{ds}$  with  $V_{gs}$  as a parameter
- (c)  $I_g$  as a function of  $V_{gs}$  with  $V_{ds}$  as a parameter
- (d)  $I_g$  as a function of  $V_{ds}$  with  $V_{gs}$  as a parameter

Q7

What is the value of common-mode gain for an ideal op-amp?

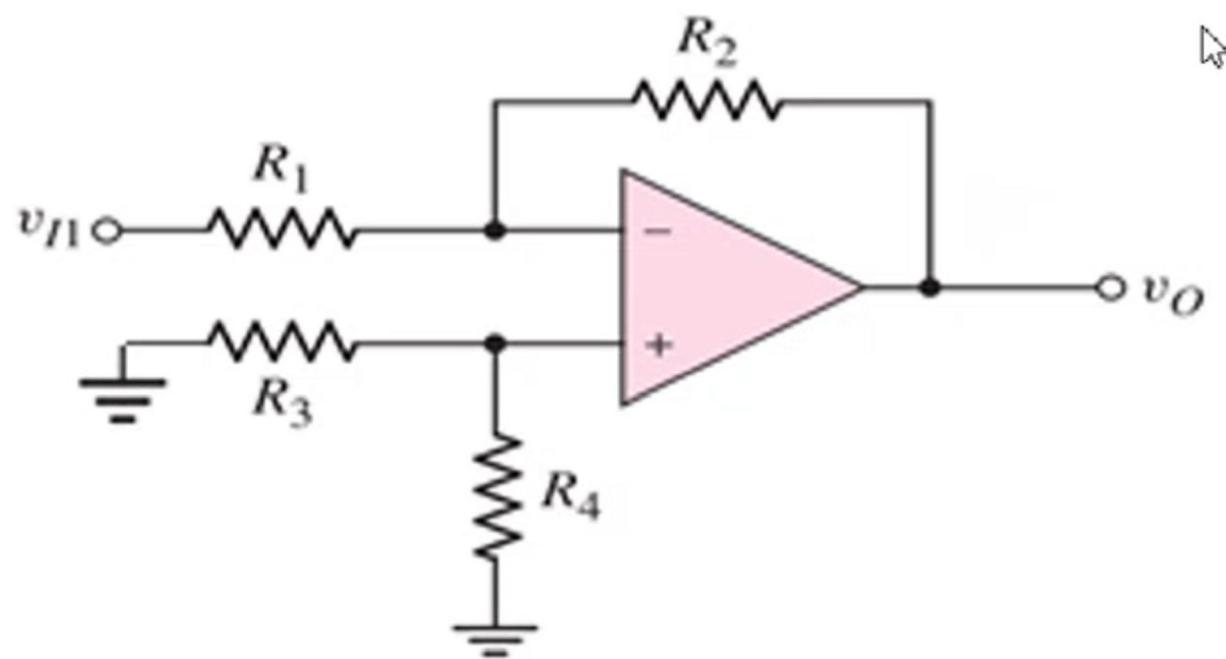Q8

What is the output voltage (in terms of resistances)





Q3

Most of the carriers flowing through the base of a BJT are majority carriers or minority carriers?

Q1

If for a BJT, the common base current gain is 0.98, then what is the value of its common emitter current gain?

Q2

Why do we use an emitter resistance in a common emitter biasing configuration?

### Q3

The BJT small signal output impedance  $r_o$  accounts for

- (a) change in  $i_c$  with  $v_{CE}$  in the active regime
- (b) change in  $i_c$  with  $v_{CE}$  in the saturation regime
- (c) change in  $i_b$  with  $v_{BE}$  in the active regime
- (d) change in  $i_b$  with  $v_{BE}$  in the saturation regime