
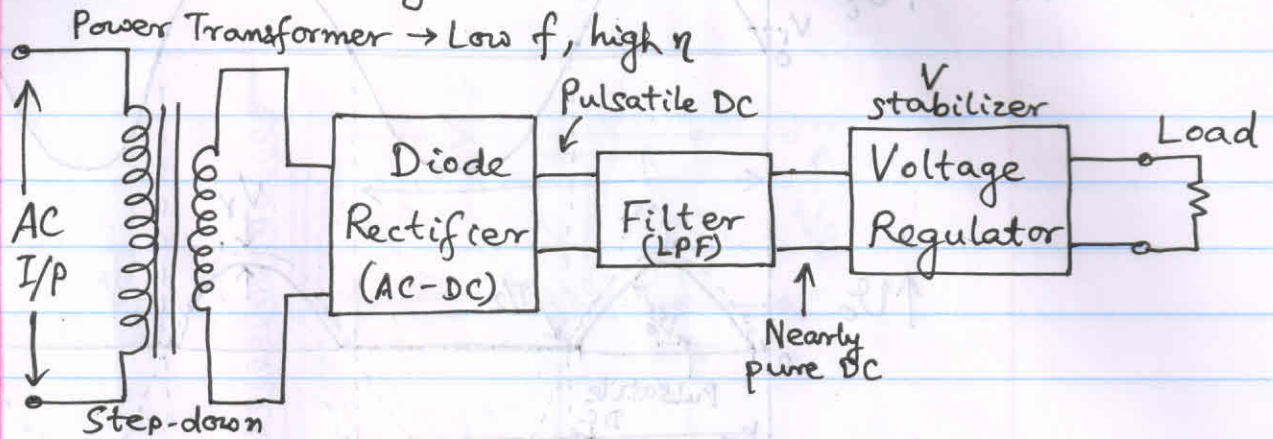


Diode Circuits

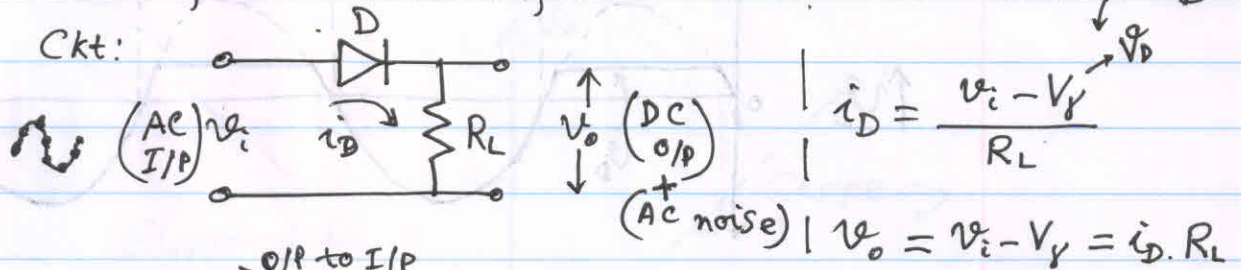
1. Power Supply architecture (^{DC} Linear)




2. Half-wave rectifier:





V-transfer characteristics:

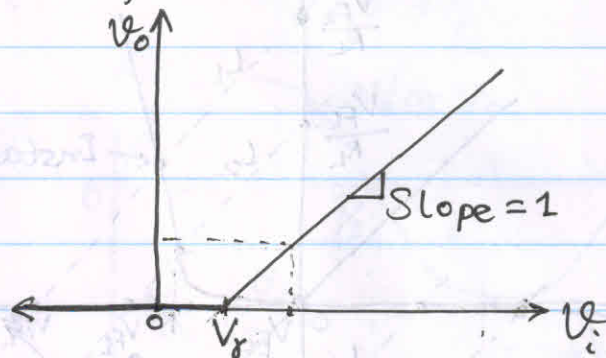




Practical ckt: Iron core

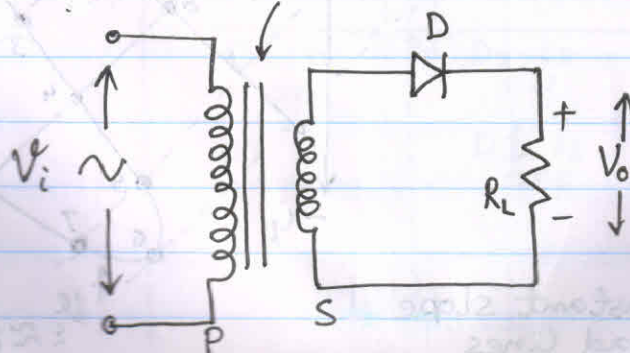

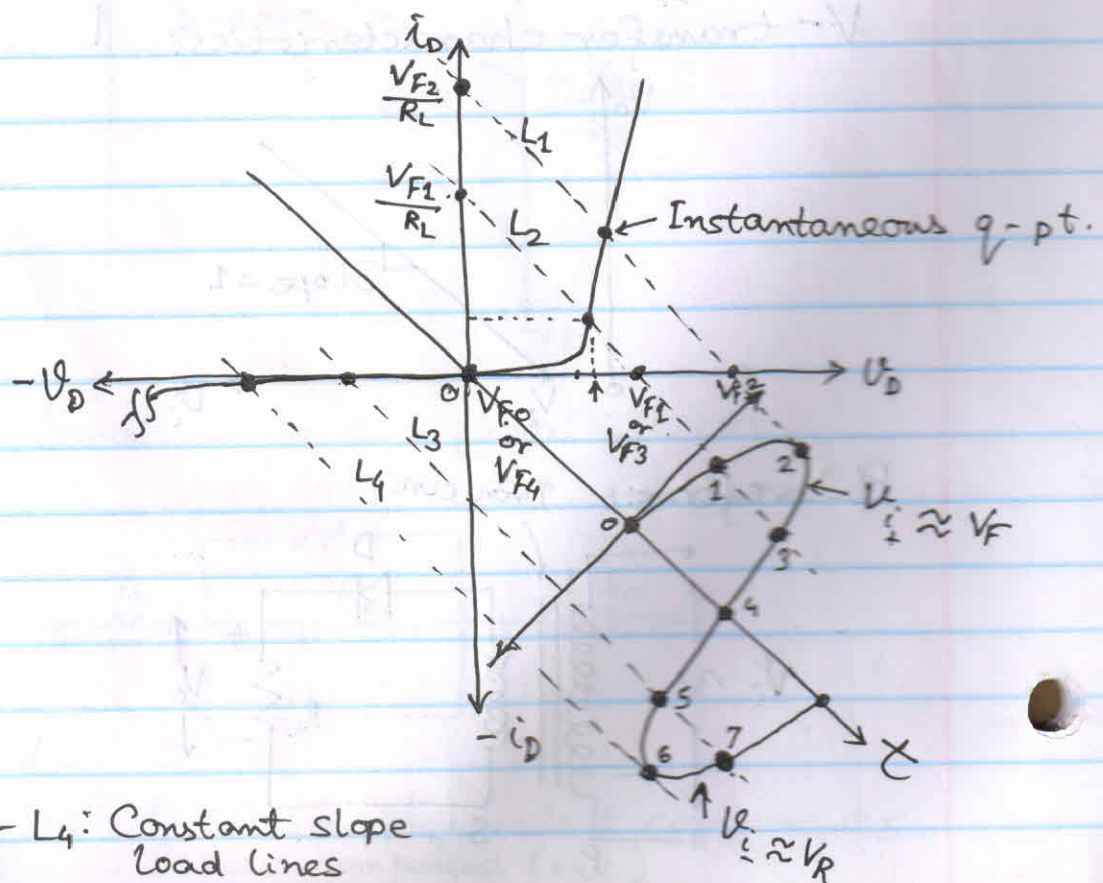
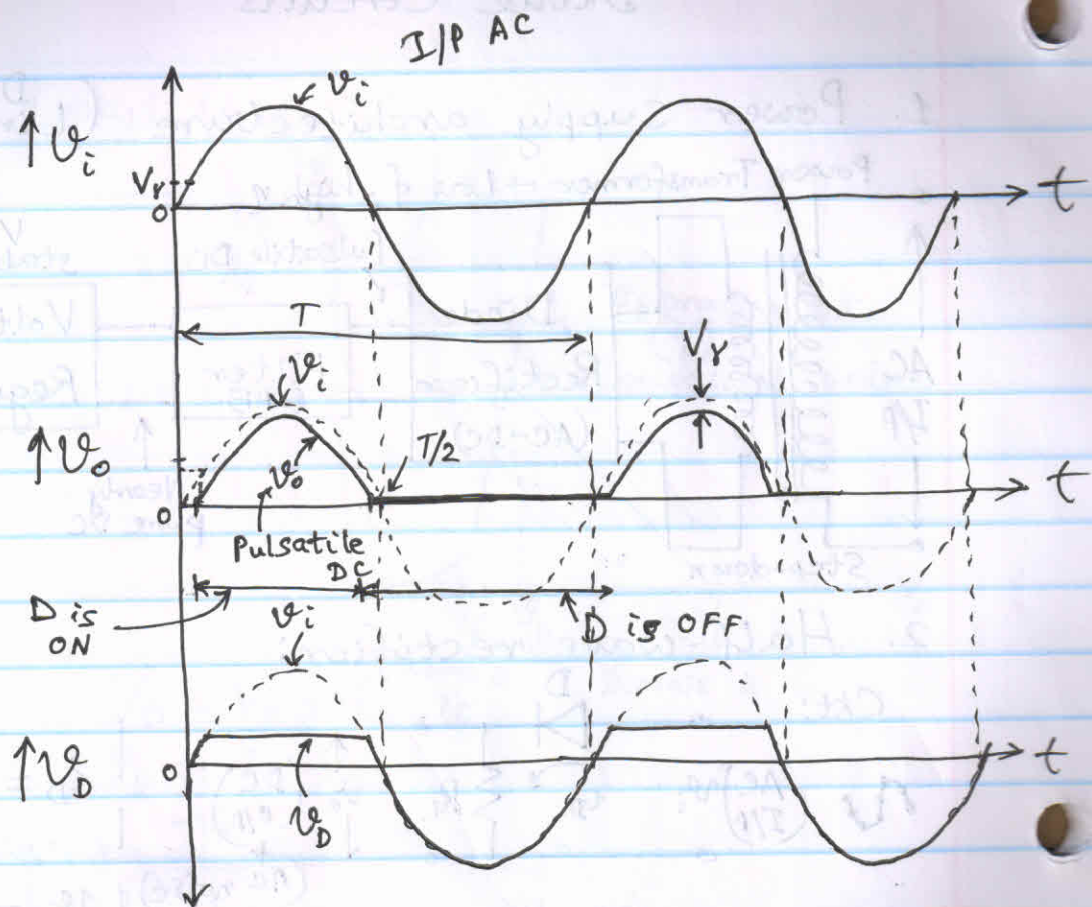


$L_1 - L_4$: Constant slope load lines


2. Full-wave rectifier:

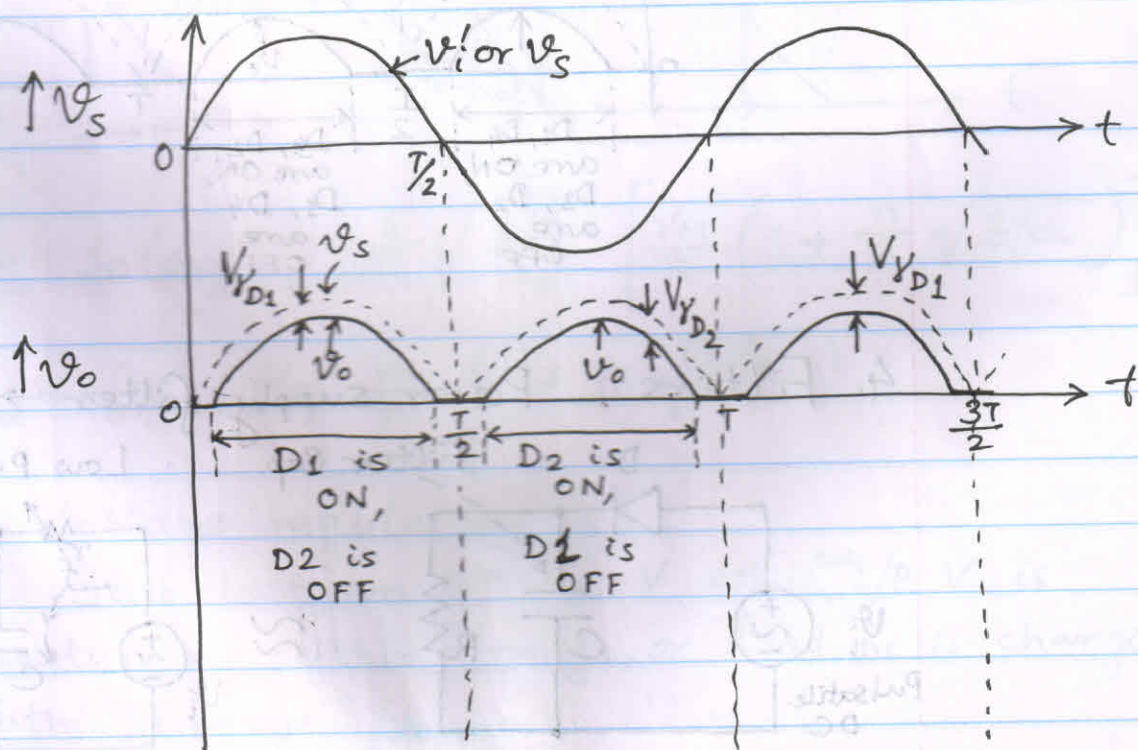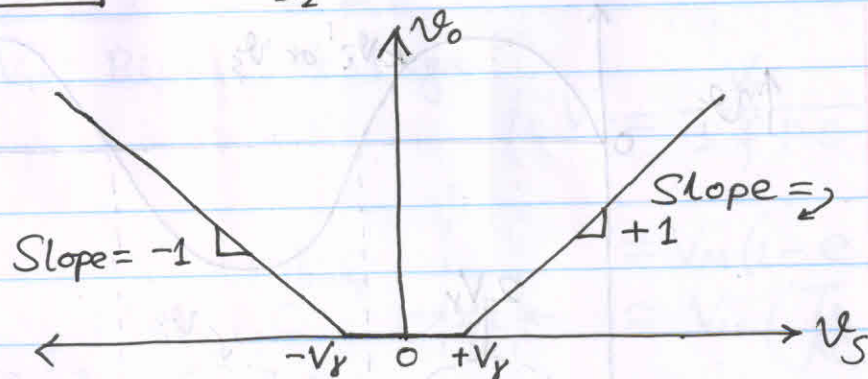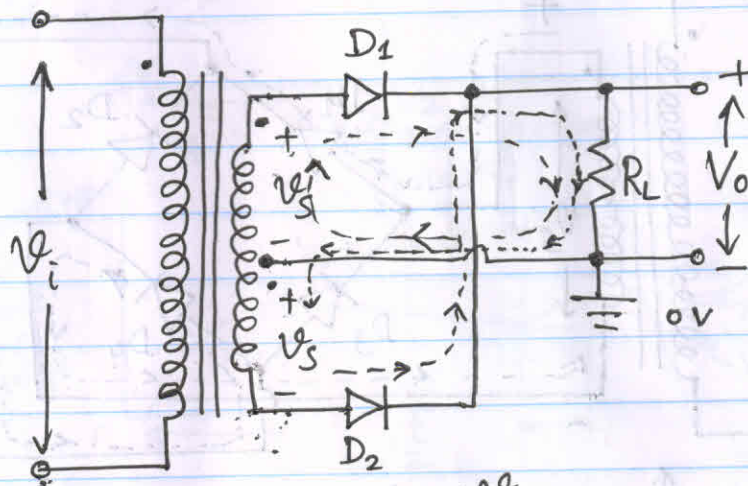


3. Bridge Rectifier:

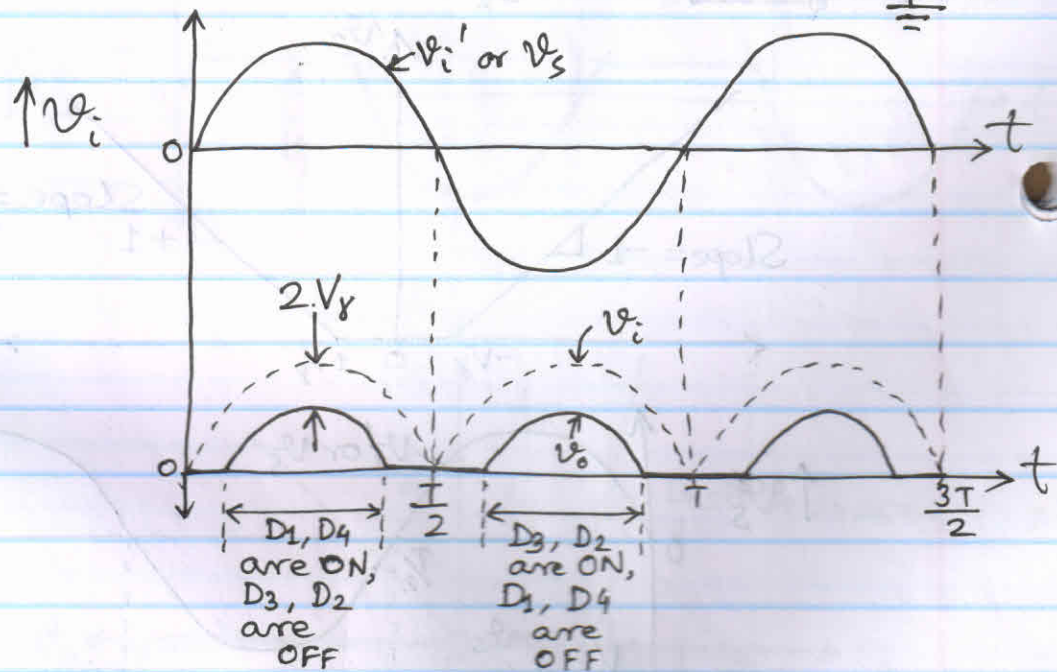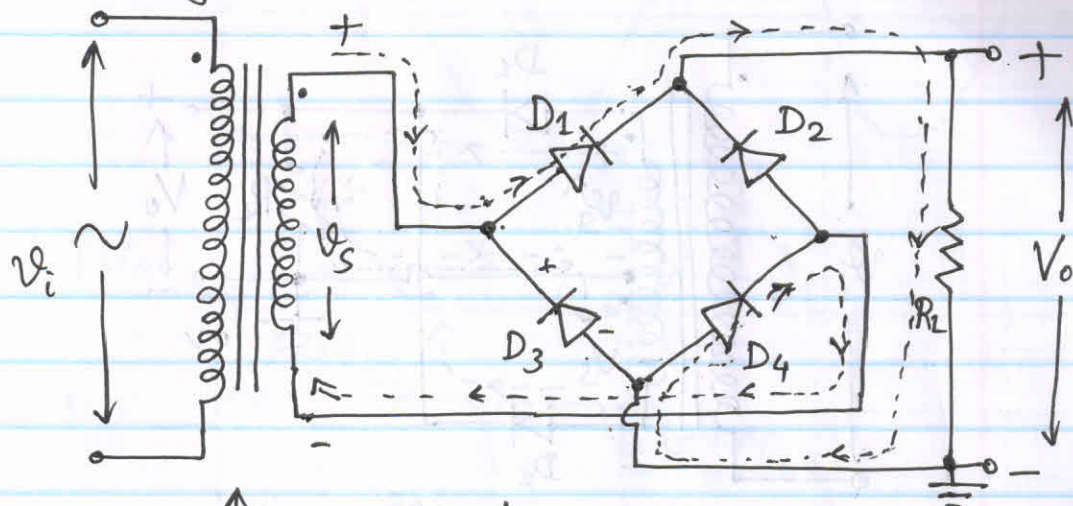

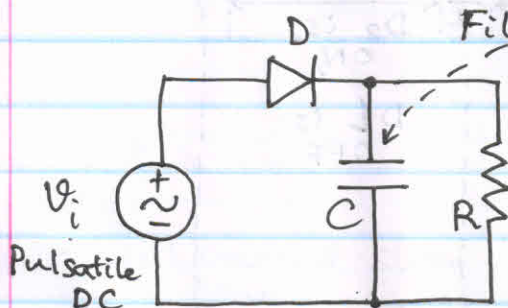
4. Filters: Power supply filter \rightarrow LPF or Low Pass Filter



\approx

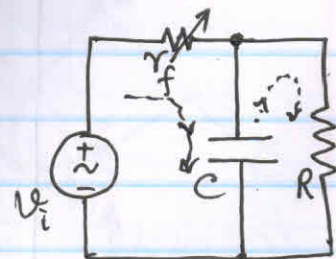
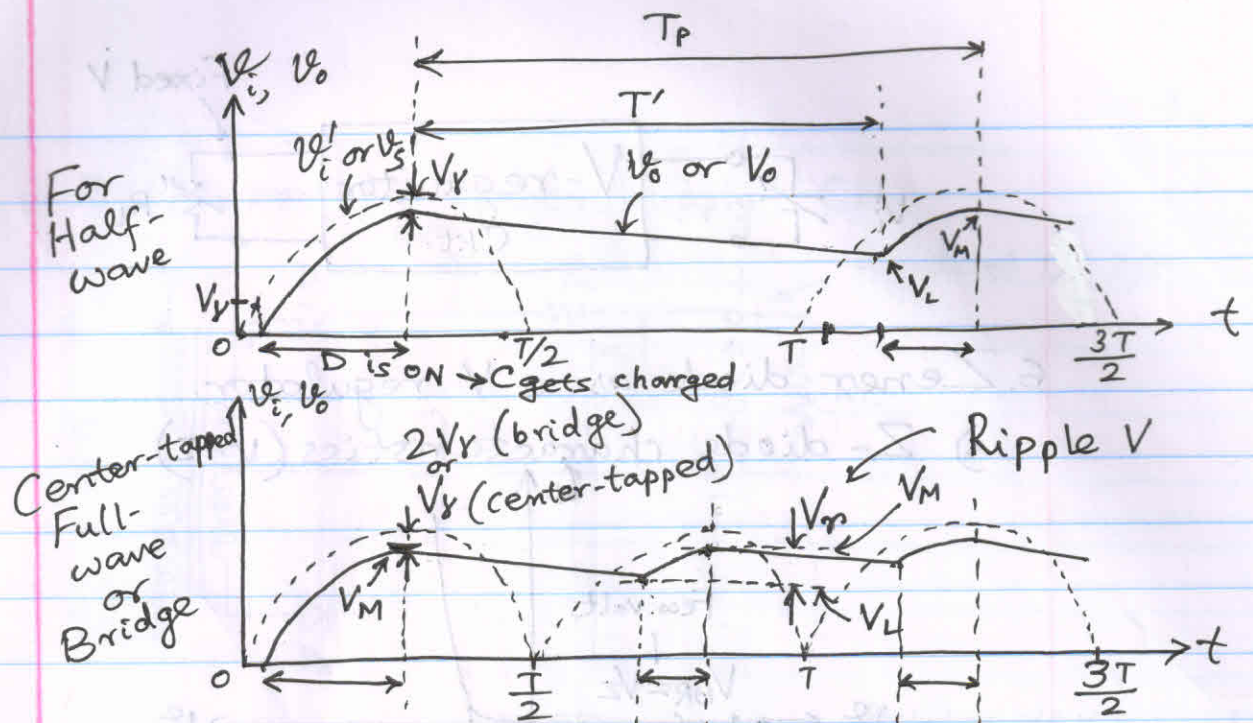
$$\begin{aligned} r_f &\approx 0 \text{ (FB)} \\ r_f &\approx \infty \text{ (RB)} \end{aligned}$$




V_r : Ripple Voltage

$$V_r = \frac{V_M}{2fRC} = V_M - V_L$$

$$= V_M(1 - e^{-\frac{T'}{RC}})$$
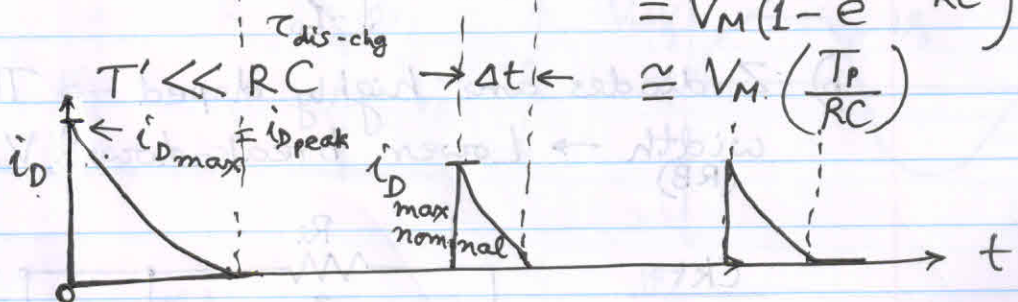
$$\cong V_M \left(\frac{T'}{RC} \right)$$




$$i_D(\text{avg.}) = \frac{1}{\pi} \sqrt{\frac{2V_r}{V_M}} \cdot \left[\frac{V_M}{R} \cdot \left(1 + \frac{\pi}{2} \sqrt{\frac{2V_M}{V_r}} \right) \right]$$

$$i_{Dmax} \cong i_D(\text{peak}) = \frac{V_M}{R} \cdot \left(1 + \pi \cdot \sqrt{\frac{2V_M}{V_r}} \right)$$

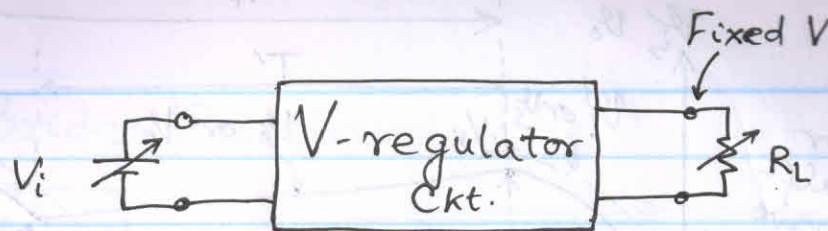
5. Voltage regulator:

Stabilizes an O/P DC V while ^{an}I/P V is fluctuating within a range, or Load R_L is changing within a range.




6. Zener diode as a V-regulator.

a) Z-diode characteristics (V-I)

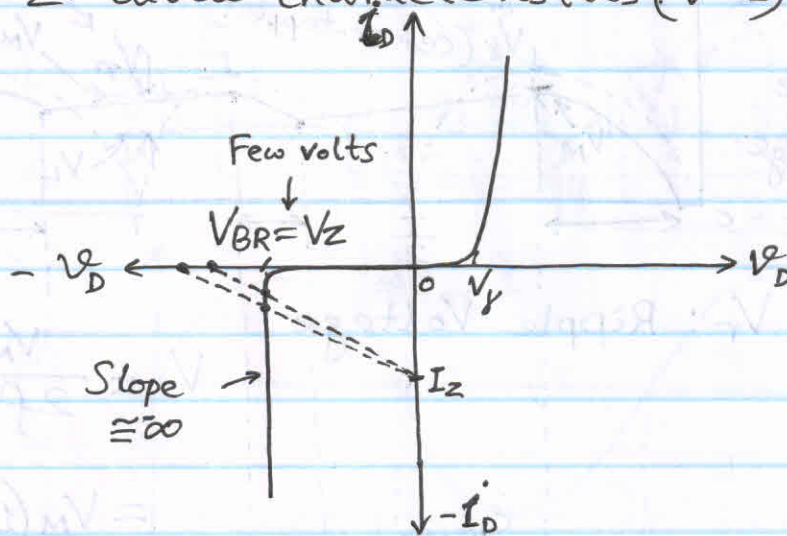

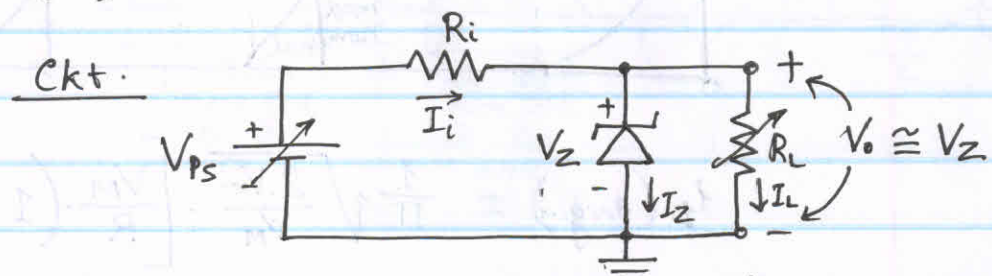b) Z-diodes are highly doped \rightarrow Thinner juncⁿ width \rightarrow Lower break-down V. (RB)




$$R_i = \frac{V_{PS} - V_Z}{I_i} = \frac{V_{PS} - V_Z}{I_L + I_Z} \quad \left| \quad I_Z = \frac{V_{PS} - V_Z}{R_i} - I_L \right.$$

$$R_i = \frac{V_{PS_{min}} - V_Z}{I_{Z_{min}} + I_{L_{max}}} \approx \frac{V_{PS_{max}} - V_Z}{I_{Z_{max}} + I_{L_{min}}}$$

$$P_Z = V_Z \cdot I_Z \quad \left| \quad I_{Z_{min}} = \frac{V_{PS_{min}} - V_Z}{R_i} - I_{L_{max}} \right.$$

7. Linear DC power supply: Ckt.

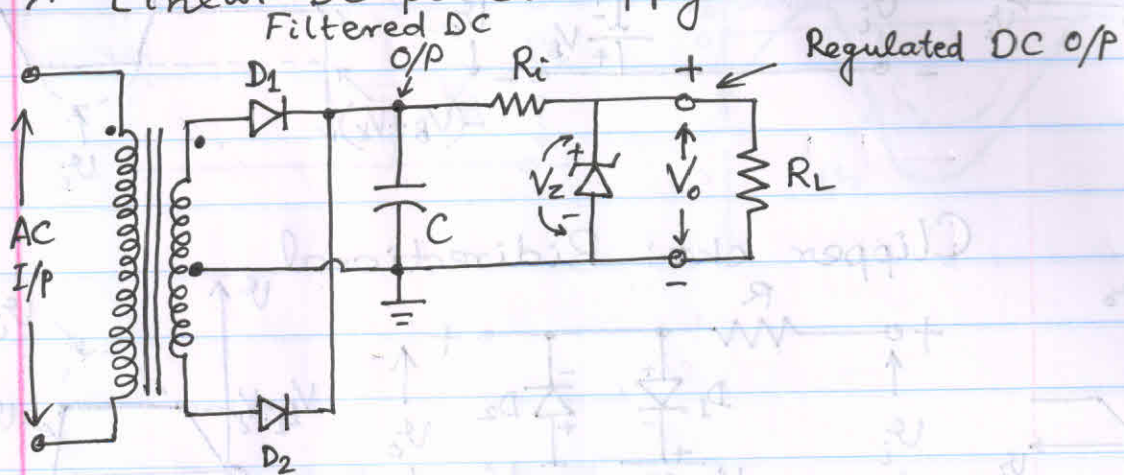

8. Clipper & Clampers (Voltage limiter ckt.).

a) Clipper ckt: Uni-directional:

