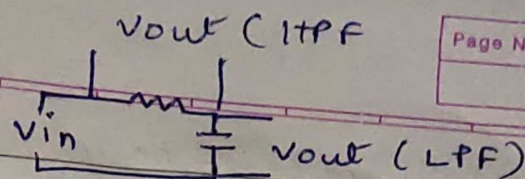


$$1.602 \times 10^{-19} = q$$



Low pass filter



$$A = \left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{R^2 \omega^2 C^2 + 1}}$$

$$V_{out}(t) \approx \frac{1}{RC} \int V_{in}(t) dt$$

when $\omega RC \gg 1$

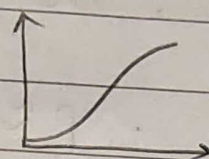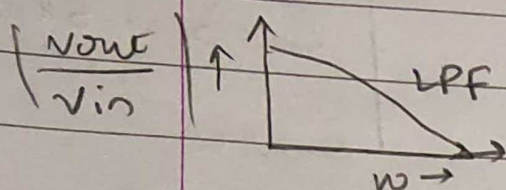

High pass filter

$$A = \left| \frac{V_{out}}{V_{in}} \right| = \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}}$$


$$V_{out}(t) \approx RC \frac{d}{dt} (V_{in}(t))$$

when $\omega RC \ll 1$

Cutoff frequency

At $\omega = \omega_c$


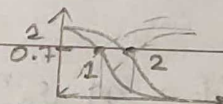
$$A = 1/\sqrt{2} \approx 0.7 \Rightarrow \omega_c = 1/RC, f_c = \frac{1}{2\pi RC}$$



$$\omega_{c1} < \omega_{c2}$$


$$R_1 C_1 > R_2 C_2$$

Band Pass Filter

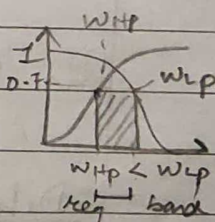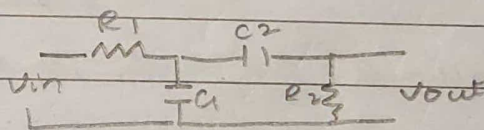

Thevenin's Theorem

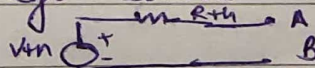- V_{th} = Open circuit voltage about req. pts
- R_{th} = voltage source \rightarrow short circuit, current \rightarrow open circuit



Semiconductors: valence band (full) | conduction band (empty) \rightarrow OK | Discrete Energy states

VB \rightarrow shifting bonds (holes) | CB \rightarrow free bonds (electrons)

1 broken bond = 2 holes

- No of holes in VB = No of e^- in CB

Band gap \sim sev at Room temp.

$$p_i = n_i$$

Dependent on material

• Non doped (Intrinsic)

• Doped (Extrinsic)

 \rightarrow n-type (Group V)
 \rightarrow p-type (Group III)

 $\rightarrow e^-$ added
 \rightarrow holes added

 $N_D \gg n_i \rightarrow$ conc. of intrinsic e^- , $n \approx N_D$
 conc. of doped donor

 $N_A \gg p_i$
 conc. of doped acceptor
• $p \approx N_A$

$$n \times p = n_i p_i$$

for Si at 300K

$$n_i = p_i = 1.5 \times 10^{10} / \text{cm}^3$$

Note

If $N_D > N_A$,
 $n = N_D - N_A \rightarrow$ n-type

 mixed-type
 (compensation doping)
Drift current :- (p-n junction)
 Mobility of e^- /holes :- $v_d^n = -\mu_n \times E$, $v_d^p = \mu_p \times E$
 velocity \downarrow field \downarrow
 opposite term

$$J_{\text{drift}} = n v_d^n (-q) + p v_d^p (+q) = J_{\text{drift}} / \text{Area}$$

$$J_{\text{drift}} = (q n \mu_n + q p \mu_p) E = \sigma E$$

\rightarrow conductivity


Force = qE , $a = qE/m$, $vel \rightarrow \text{const}$, $a \rightarrow 0$ Diffusion current :-

$$J_{\text{diff}}^n = q D_n \nabla n$$

\downarrow spatial gradient
Diff. coeff of e^-

$$J_{\text{diff}}^p = q D_p (-\nabla p)$$

$$J_{\text{diff}} = J_{\text{diff}}^n + J_{\text{diff}}^p$$

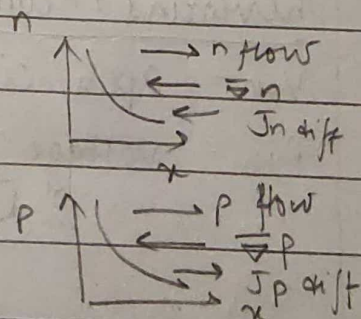Diff coeff \propto speed of diff. of e^- /holes respectively


Assume:- $n = A e^{-\alpha x} \Rightarrow \nabla n = \frac{\partial n}{\partial x} \hat{i} + \frac{\partial n}{\partial y} \hat{j} + \frac{\partial n}{\partial z} \hat{k} = -A \alpha e^{-\alpha x} \hat{i}$

$$|I_{diff}| = |I_{drift}| \Rightarrow \text{total } I = 0$$

- Equilibrium :- No external source of excitation except temp.
No current/voltage source applied, No flow of I


Law of Mass Action :- Only valid in Equilibrium

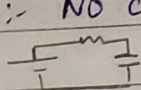- Steady State :- No change in device measurables with time



P-n junction
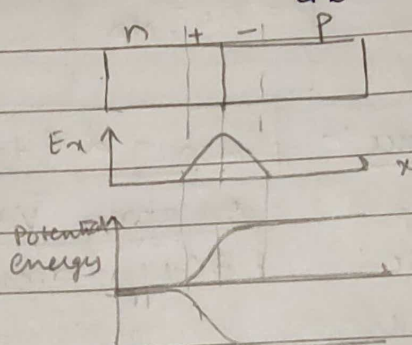
$$\nabla \cdot \vec{E} = \frac{dEx}{dx} = \frac{\rho}{\epsilon} \rightarrow \begin{matrix} \text{electric field} \\ \text{accumulated} \\ \text{charge density} \\ \text{Permittivity} \end{matrix}$$



$$\rho > 0, Ex \uparrow$$

$$\rho < 0, Ex \downarrow$$


potential energy seen by e^-

V_{bi} actual PE

$$V_{bi} = V_{built-in} = \frac{kT}{q} \ln \frac{N_A N_D}{n_i^2}$$

Forward Bias

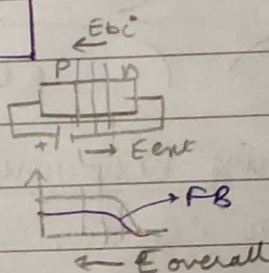- $I_{diffusion} \uparrow$
- I_{drift} doesn't change



diff e^-
drift holes
drift e^-
diff holes

$$I = I_{drift} + I_{diff} = I_s \left(e^{\frac{V}{nV_T}} - 1 \right)$$

diffusion drift


material dependent

$$V_T = \frac{kT}{q} \approx 25.9 \text{ meV}$$

at $T = 300K$

η = ideality factor
1 to 2
ideal p-n junc

FB characteristics

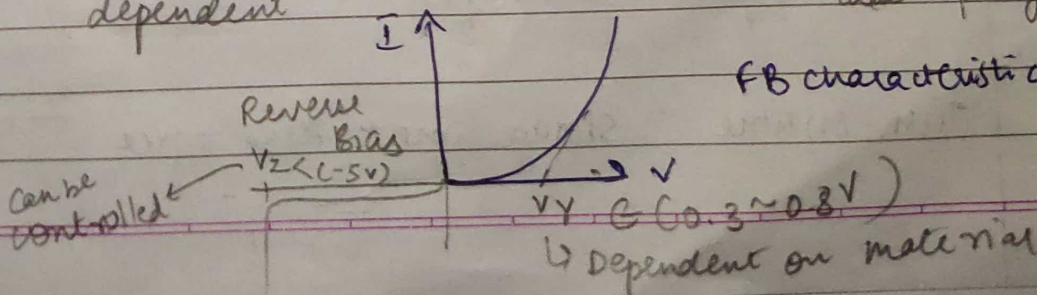

FABER-CASTELL
since 1761
Art Canvas

FABER-CASTELL
since 1761
Art Canvas


FABER-CASTELL
since 1761
Art Canvas

STELL
Canvas

Reverse Bias

$$I = I_s (e^{\frac{V}{V_T}} - 1)$$

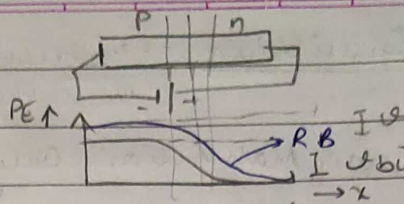$\approx I_s$ (reverse saturation current)



Breakdown:- High E breaks bonds to release e⁻-hole pair

Minority carriers:-

n-type SC $p = n_i^2 / N_D$	p-type semiconductor $n = n_i^2 / N_A$
--------------------------------	---

Depletion Capacitance:-

$$C_{dep} = dQ_{dep} / dV$$

(in depletion region)



On apply VAC || due to oscillation of depletion region

Diffusion Capacitance:-

$$C_{diff} = dQ_{diff} / dV$$

(outside depletion region)

due to oscillation of minority charges

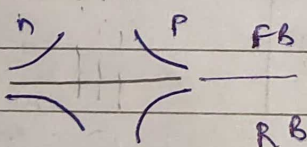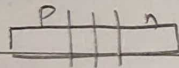


on application of VAC (minority charge conc. # on either side)

Equilibrium

Switching behaviour of p-n junction


FB to RB switch at $t=0$

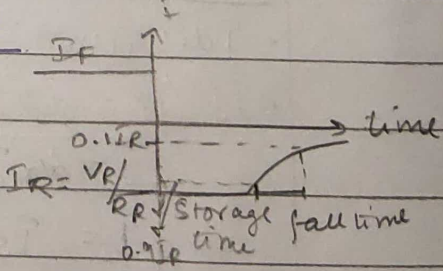due to previously accumulated excess minority charges




Turn-off time = storage time + fall time
(time eq. for FB to RB shift)

Turn-on time = storage time + rise time

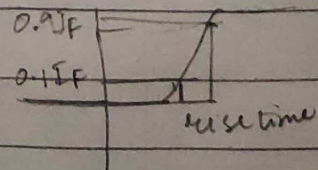

Piecewise linear model

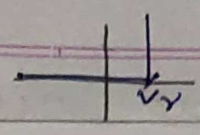

$V < V_r, I = 0$
 $V > V_r, dI/dV \rightarrow \infty$

(when current flows through the diode, $V_D = V_r$)

Small signal AC model



$g_d = I_{DC} / V_T$

$25.9 \text{ mV at } T = 300 \text{ K}$

equivalent resistance = g_d^{-1}
 for AC voltage



g_d^{-1}
 for low/mod. freq.
 high freq.

Load Line Analysis

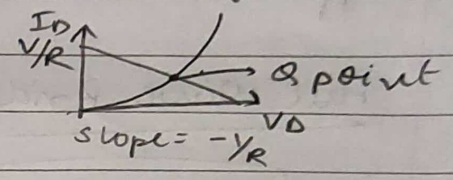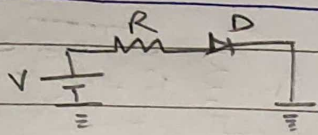



Transformer : $V_{in} \text{ (primary)} = \frac{N_1}{N_2} \rightarrow \text{primary turns}$
 $V_{out} \text{ (secondary)}$

Half-wave rectifier :

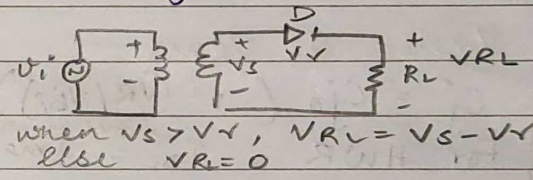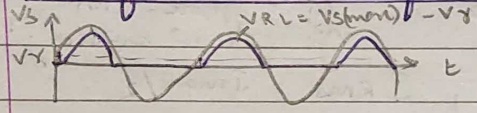

when $V_S > V_r$, $V_{RL} = V_S - V_r$
 else $V_{RL} = 0$

With capacitive filter

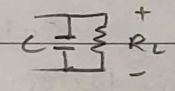
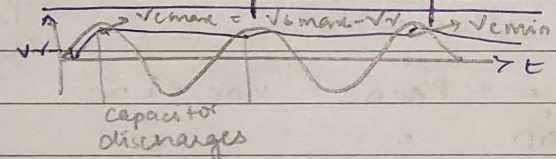


$V_D = V_S - V_{C \text{ max}}$
 $\leq V_{S \text{ max}} - V_{C \text{ max}}$
 $V_D \leq V_r$ (only when $V_{S \text{ max}}$)

$PIV = V_{S \text{ max}}$ (without capacitor) always +ve
 $= \frac{1}{2} (2V_{S \text{ max}} + V_r)$ (with capacitor)

* $V_{\text{ripple}} = V_{\text{max}} - V_{\text{min}} = T_P / C R_L$
 T_P :- Time period of V_S
 R_L :- Load
 C :- Capacitance

Full wave rectifier : (Center tapped)

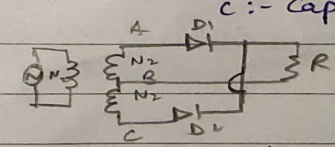
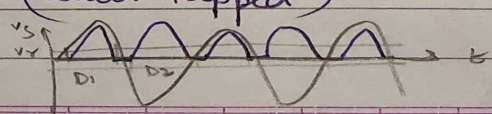


$V_{RL \text{ max}} = V_{S \text{ max}} - V_r$

+ve cycle
 $V_A > V_B > V_C$
 -ve cycle
 $V_A < V_B < V_C$

$PIV = 1 - V_r + 2V_{S \text{ max}}$

Page No.:

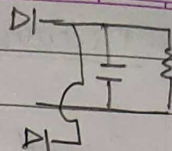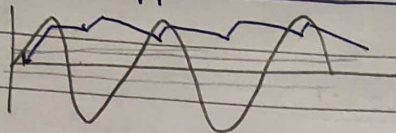Centre tapped with capacitor


$$V_{\text{ripple}} = V_{C_{\text{max}}} - V_{C_{\text{min}}} = (T/2) V_{C_{\text{max}}} / RLC$$

Time period of capacitor = $\frac{1}{2}$ of time period

Full Wave Bridge Rectifier

$$PIV = V_{S_{\text{max}}} - V_r$$
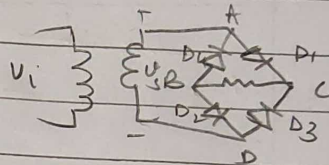
$$R_{L_{\text{max}}} = V_{S_{\text{max}}} - 2V_r$$



$$V_{\text{max}} = \sqrt{2} V_{\text{RMS}}$$

$$C_j = C_{j0} \left(1 + (V_r / V_{bi}) \right)^{-1/2}$$

$$\text{For HWR, } I_{DC} = I_{\text{max}} / \pi$$

$$I_{\text{RMS}} = I_{\text{max}} / 2$$

when RB voltage is applied

C_j :- junction capacitance
 C_{j0} :- zero biased junction cap.

$V_{ac(RMS)}$
 V_{dc}

$$\text{Output } V_{DC} = I_{DC} \times R_L$$

$$\text{Ripple factor } r = \frac{I_{ac}}{I_{DC}} = \frac{(\sqrt{I_{\text{RMS}}^2 - I_{DC}^2})}{I_{DC}} \rightarrow \text{lower ripple factor} \rightarrow \text{good power supply}$$

$$\text{Power (ac)} = P_{\text{RMS}} \quad \text{or} \quad P_{\text{DC}} = V_{DC} \times I_{DC}$$

$$\text{efficiency } = \eta = \frac{P_{\text{DC}}}{P_{\text{AC}}} \times 100 = \frac{\text{output}}{\text{input}} \times 100$$

$$n_i = 1.5 \times 10^{10} / \text{cm}^3 = B T^{3/2} e^{\left(\frac{-E_g}{2kT} \right)}$$

at $T = 300 \text{ K}$

$$\text{minority carrier hole conc.} = n_p e^{\left(\frac{V_{\text{applied}}}{kT} \right)}$$

equilibrium conc.