

19MA20059

Keerti P. Chavanmath

Basic EC - Test 4

---

---




19MA20059


Keerthi P. Chakraborty

Basic EC - Test 4

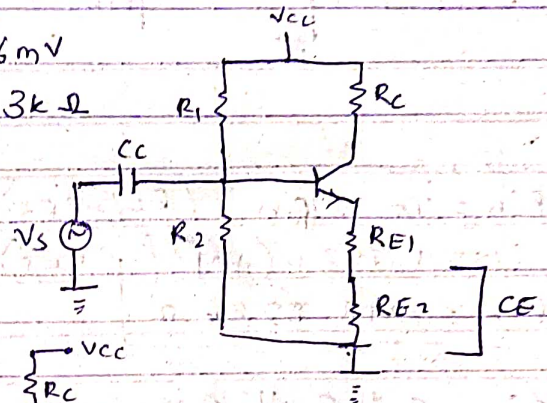Q4)  $\beta = 100$   $V_{BE(ON)} = 0.7V$   $V_T = 26mV$   
 $R_1 = 20k\Omega$   $R_2 = 10k\Omega$   $R_C = 3k\Omega$   
 $R_{E1} = 1k\Omega$   $R_{E2} = 1.1k\Omega$   
 $C_C = C_E = 10\mu F$  ,  $V_{CC} = 12V$



a) DC Analysis  
 Equivalent Circuit

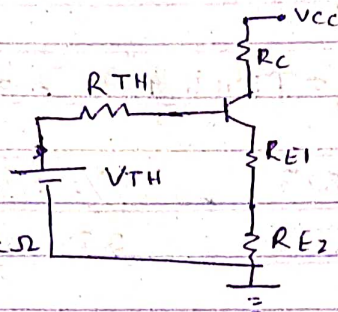

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = \frac{20 \times 10}{20 + 10} = \frac{200}{3} k\Omega$$

$$V_{TH} = \frac{R_2 (V_{CC})}{R_1 + R_2} = \frac{10 \times 12}{20 + 10} = 4V$$

$$V_{TH} = I_B R_{TH} + V_{BE(ON)} + I_E (R_{E1} + R_{E2})$$

$$4 = \frac{I_B}{\beta} \left( \frac{200}{3} \right) + 0.7 + (1.1 + 1)(100) \frac{I_B}{\beta}$$

$$4 - 0.7 = 218.766 I_B \Rightarrow I_B = 0.01508 mA$$


Now  $r_{\pi} = \frac{V_T}{I_B} = \frac{26mV}{0.01508mA} = 1723.6\Omega = 1.723k\Omega$

$$g_m = \frac{\beta}{r_{\pi}} = \frac{100}{1.723k\Omega} = 58.017 \text{ millimho}$$



19MA20059

b)  $V_A = \infty \Rightarrow h_o = 0$

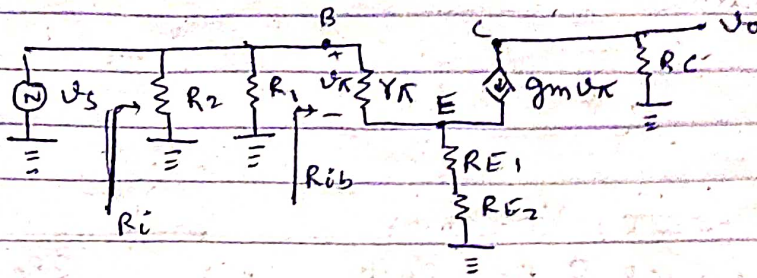

$R_1 = 20k\Omega$

$R_2 = 10k\Omega$

$R_{G1} = 1k\Omega$

$R_{E2} = 1.1k\Omega$

$r_K = 1.723k\Omega$

$g_m = 58.017$   
milli-mho

$R_L = 3k\Omega$

$$R_{ib} = r_K + (\beta + 1)(R_{E1} + R_{E2})$$

$$= 1.723 + (101)(1.1 + 1)$$

$$R_{ib} = 213.823k\Omega$$

$$R_i = R_1 \parallel R_2 \parallel R_{ib} = R_{TH} \parallel R_{ib} = \frac{20}{3} \parallel 213.823$$

$$= \frac{\frac{20}{3} \times 213.823}{\frac{20}{3} + 213.823} = \frac{20/3 \times 213.823}{220.489}$$

$$R_i = 6.465k\Omega$$

c) CE not connected

$$\frac{V_s}{R_i} = I_b \Rightarrow I_b = \frac{V_s}{R_i}$$

$$V_K = I_b r_K = \frac{V_s r_K}{R_i} = \frac{V_s (1.723)}{(213.823)} = V_s (8.058 \times 10^{-3})$$

$$g_m V_K = (58.017) V_s (8.058 \times 10^{-3}) \text{ milli-mho-volt}$$

$$= 467.5009 V_s \times 10^{-3} \text{ mA}$$

$$O - V_o = g_m V_K R_C = 467.5009 \times 3 V_s$$

$$- V_o = 1402.5029 V_s \text{ mV}$$

$$V_o = -1.4025 V_s \text{ mV}$$

$$\text{Gain } A_v = \frac{V_o}{V_i} = \frac{-1.4025 V_s}{V_s} = -1.4025$$



19MA20059


When CE is connected,  $R_{ib}$  decreases as  $R_{E2}$  is bypassed in AC circuit.

As a result  $v_{\pi}$  increases. Hence  $i_c = g_m v_{\pi}$  also increases

Due to increase in  $g_m v_{\pi}$ , overall voltage gain of the circuit  $(A_v = \frac{v_o}{v_i})$  increases.

Hence, attaching capacitor CE results in increase of voltage gain

Q3)

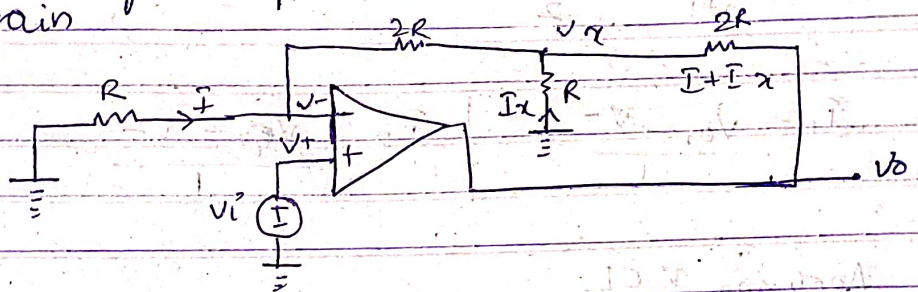

$$V_+ = V_i$$

~~Since the op-amp is ideal,  $V_- = V_+ = V_i$ .~~

$$V_- = V_+ = V_i \quad (\text{Virtual ground})$$

$$I = \frac{-V_-}{R} = \frac{-V_i}{R}$$

$$V_x = V_- - I(2R) = V_i - 2R\left(\frac{-V_i}{R}\right) = 3V_i$$

$$I_x = \frac{-V_x}{R} = \frac{-3V_i}{R}$$

$$I + I_x = \frac{-V_i}{R} - \frac{3V_i}{R} = \frac{-4V_i}{R}$$


$$\text{Now } V_o = V_x - (I + I_x)2R = 3V_i - 2R\left(\frac{-4V_i}{R}\right) = 3V_i + 8V_i$$

$$V_o = 11V_i$$

$$\boxed{\text{gain} = A_v = \frac{V_o}{V_i} = \frac{11V_i}{V_i} = 11}$$



19MA20059

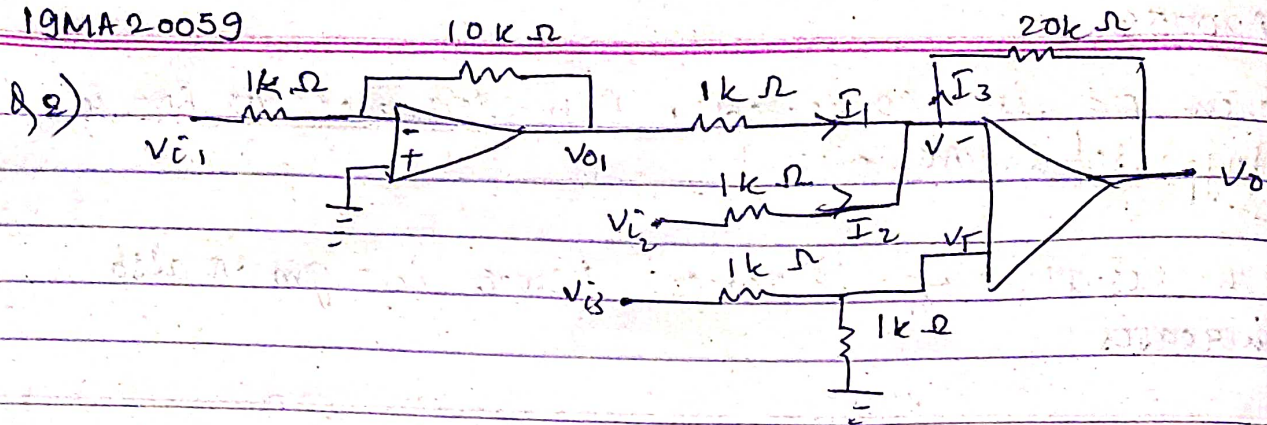

$$V_{o1} = -10V_{i1}$$

$$V_+ = \frac{V_{i3}}{1+1} = \frac{V_{i3}}{2} \approx V_-$$

$$I_1 = \frac{V_{o1} - V_-}{1} \quad \bigg| \quad I_2 = \frac{V_{i2} - V_-}{1}$$

Applying KCL

$$I_3 = I_1 + I_2 = (V_{o1} + V_{i2} - 2V_-)$$

$$\begin{aligned} V_o &= V_- - I_3 \times 20 \text{ k}\Omega = V_- - (V_{o1} + V_{i2} - 2V_-) \times 20 \\ &= 41V_- - 20V_{o1} - 20V_{i2} \end{aligned}$$

$$V_o = \frac{41}{2} V_{i3} + 200V_{i1} - 20V_{i2}$$



19MA20059

$$Q1) b) C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.9 \times 8.85 \times 10^{-12}}{8 \times 10^{-9}} = 4.3164 \text{ mF/m}^2$$

$$c) k_n' = \mu_n C_{ox} = 450 \times 10^{-4} \times 4.3164 \times 10^{-3}$$

$$k_n' = 1.9422 \times 10^{-4} \text{ F/V}$$

$$k_n = \frac{k_n' W}{2L} = \frac{1.9422 \times 10^{-4} \times 10}{2} = 9.711 \times 10^{-4} \text{ F/V}$$

$$d) I_D = k_n (V_{GS} - V_{TN})^2$$

$$100 \times 10^{-6} = 9.711 \times 10^{-4} \times (V_{GS} - 0.7)^2$$

$$= \therefore (V_{GS} - 0.7)^2 = 0.012976$$

$$\Rightarrow V_{GS} = 1.021 \text{ V}$$

a) n-channel MOSFET

$$b) V_{DS}^{(sat)} = V_{GS} - V_{TN} = 1.021 - 0.7 = 0.321 \text{ V}$$

$$\therefore V_{DS}^{(sat)} = 0.321 \text{ V}$$