

Indian Institute of Technology, Kharagpur

Date. February 22, 2021

Time: 45 mins

Full Marks: 10

Second Class Test (Spring) Semester 2020-21

Subject Name: Discrete Mathematics

Instruction: Notations used are as explained in the class.

1. [2 **mark**] Prove or disprove:

Cantor's Ternary Set \mathcal{T} where \mathcal{T} is the set of real numbers of the form

$$\frac{a_1}{3} + \frac{a_2}{3^2} + \frac{a_3}{3^3} + \cdots + \frac{a_n}{3^n} + \cdots$$

where each a_n is either 0 or 2, is not a countable set.

2. [2 **mark**] Implement the following function with two-input NAND gates. Assume that both the normal and complement inputs are available.

$$(AB + \bar{A} \bar{B})(\bar{C}D + C\bar{D})$$

3. [2 **mark**] Use the Quine-McCluskey method to simplify the *sum-of-products* expression for

$$f(x, y, z) = xy\bar{z} + x\bar{y}z + x\bar{y} \bar{z} + \bar{x}yz + \bar{x} \bar{y}z$$

4. [2 **mark**] With the use of maps, find the simplest form in sum of products of the function $F = fg$, where f and g are given by:

$$f = wx\bar{y} + \bar{y}z + \bar{w}y\bar{z} + \bar{x}y\bar{z}$$

$$g = (w + x + \bar{y} + \bar{z})(\bar{x} + \bar{y} + z)(\bar{w} + y + \bar{z})$$

5. [2 **mark**] The following Boolean expression:

$$BE + \bar{B}D\bar{E}$$

is simplified version of expression:

$$\bar{A}BE + BCDE + B\bar{C} \bar{D}E + \bar{B} \bar{C}D\bar{E}$$

Are there any don't care conditions? If so, what are they?

————The End————